

# Early Output Logic using Anti-Tokens

# Early Output Logic using Anti-Tokens


Charlie Brej  
cb@cs.man.ac.uk

Amulet Group  
Manchester University



Note: This talk > next talk


# Early Output Logic using Anti-Tokens

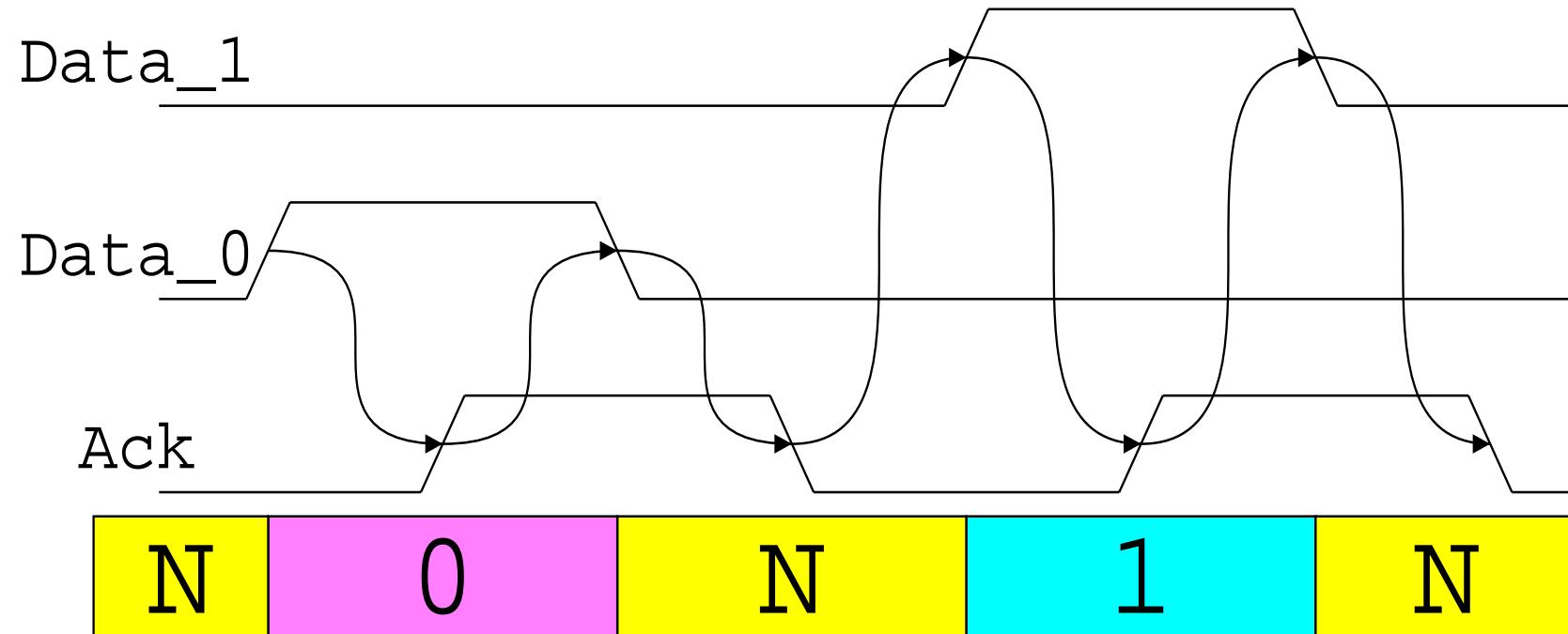

Dual-rail, four-phase, return to zero, protocol




# Early Output Logic using Anti-Tokens

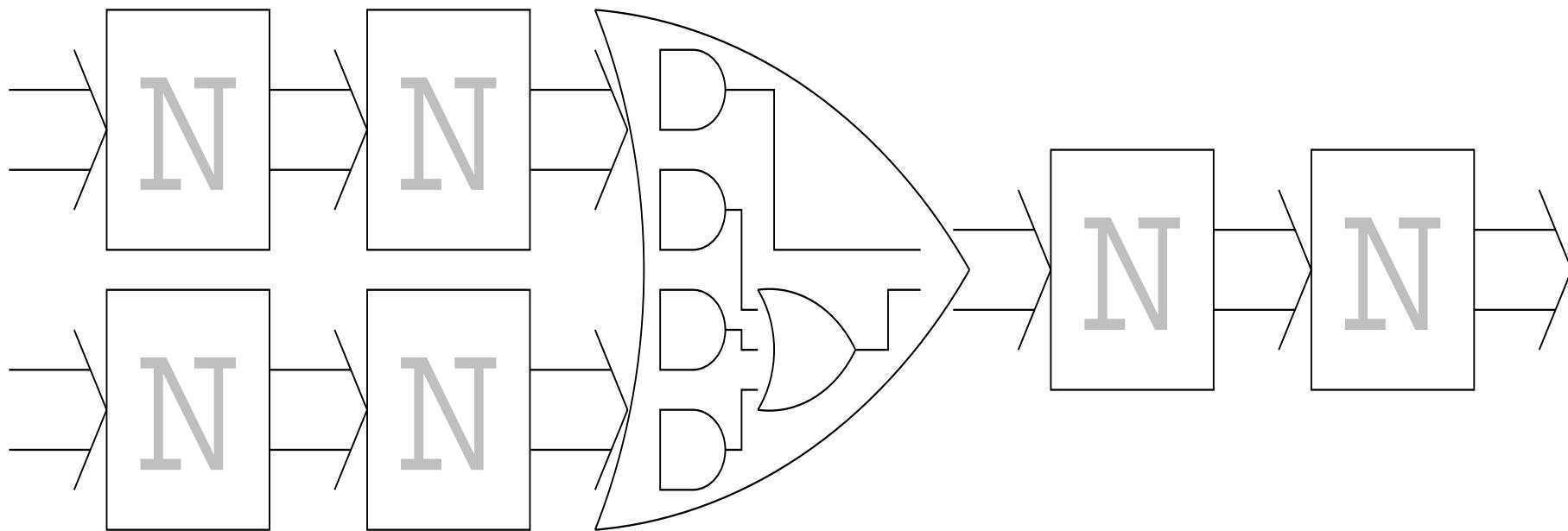


DIMS OR gate example



# Early Output Logic using Anti-Tokens

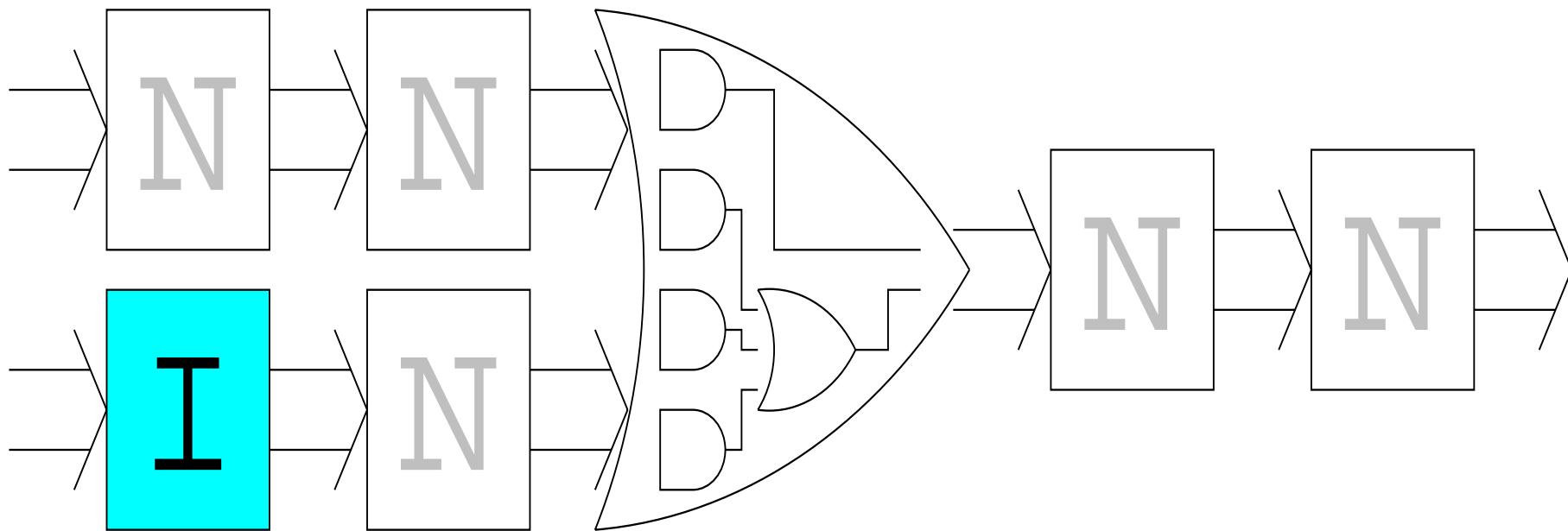


# Early Output Logic using Anti-Tokens

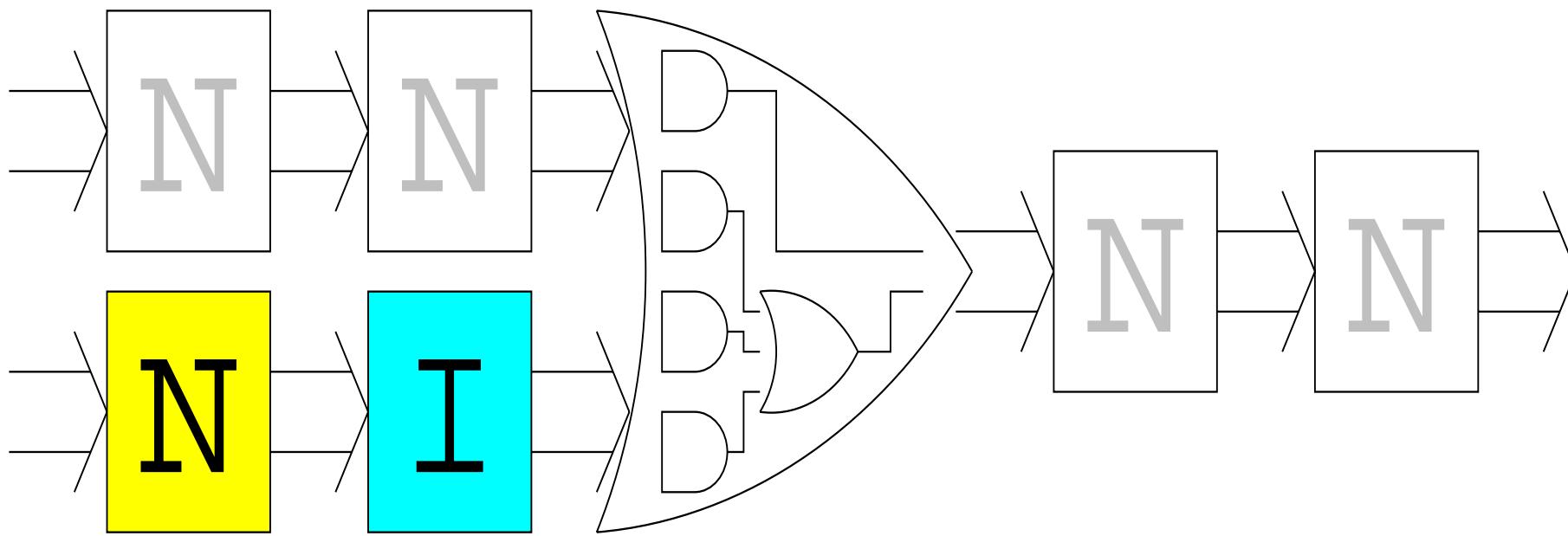

Gate stuck in set phase




# Early Output Logic using Anti-Tokens

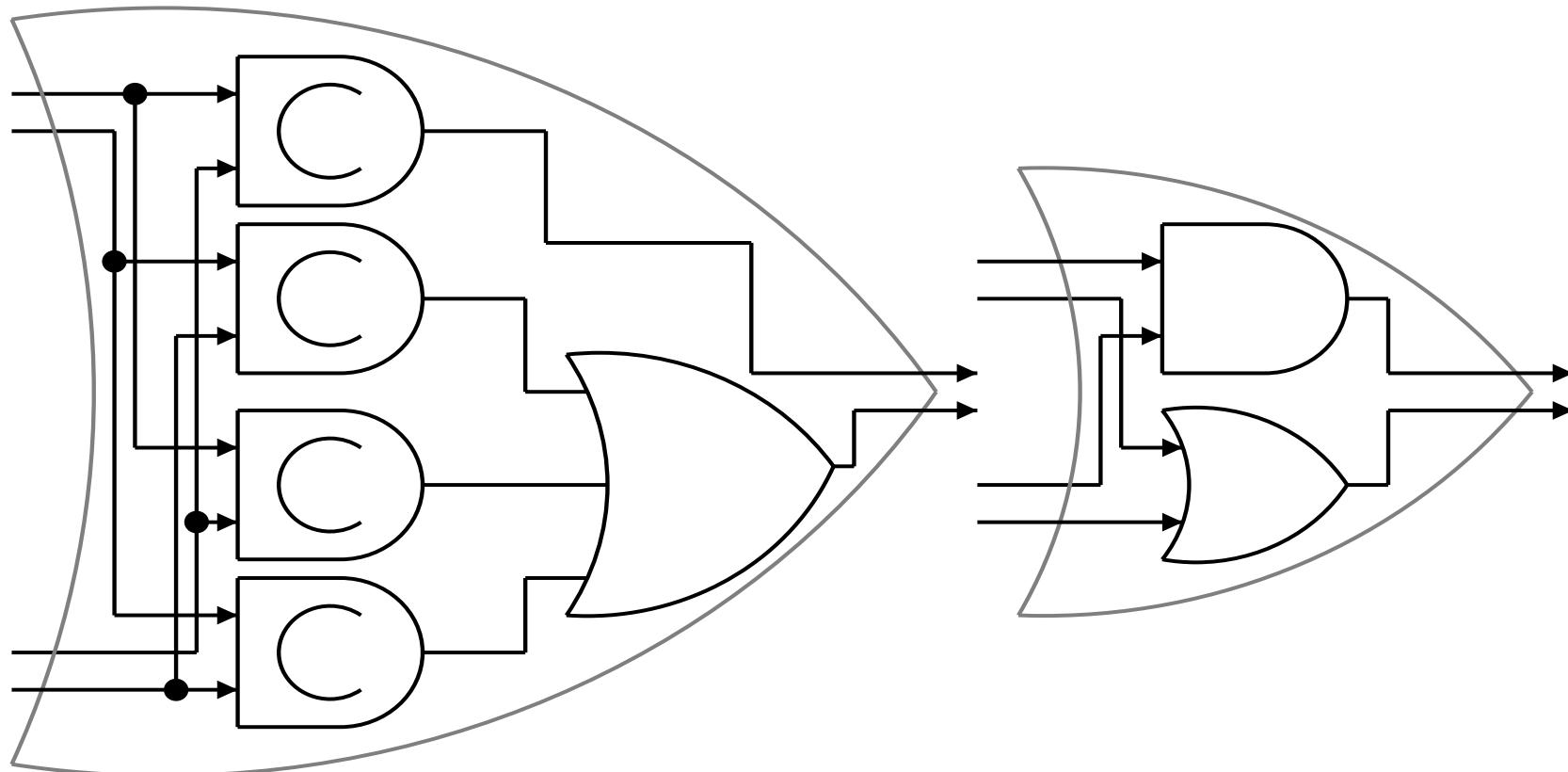

	0	N	1
0	0	N	1
N	N	N	N
1	1	N	1

	0	N	1
0	0	N	1
N	N	N	1*
1	1	1*	1

# Early Output Logic using Anti-Tokens

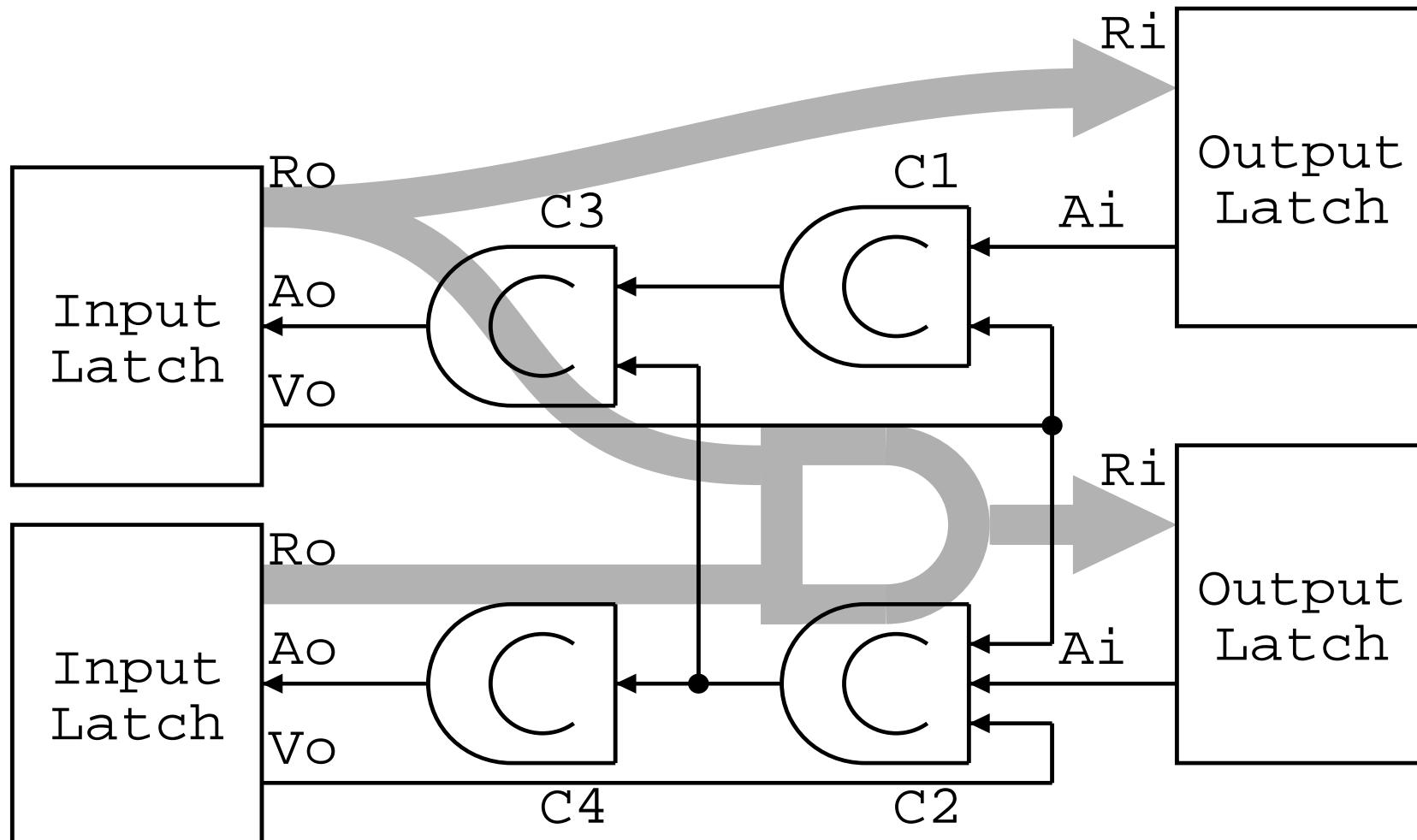


Guarding example




THE UNIVERSITY  
of MANCHESTER

# Early Output Logic using Anti-Tokens

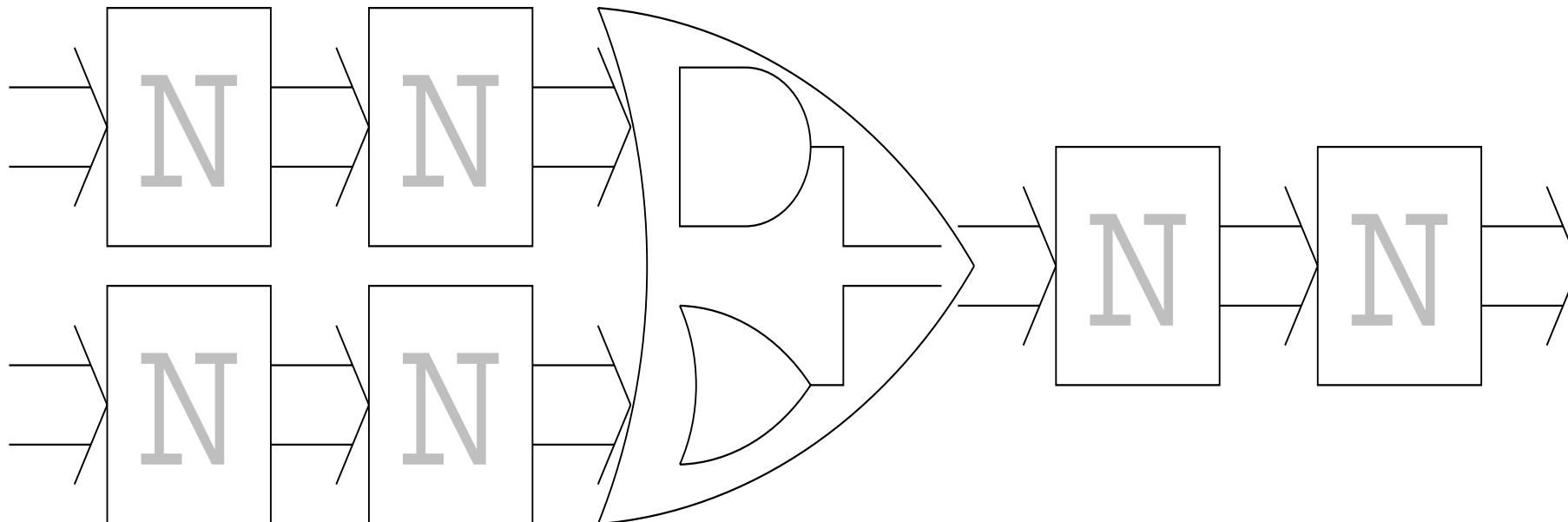


THE UNIVERSITY  
of MANCHESTER

# Early Output Logic using Anti-Tokens

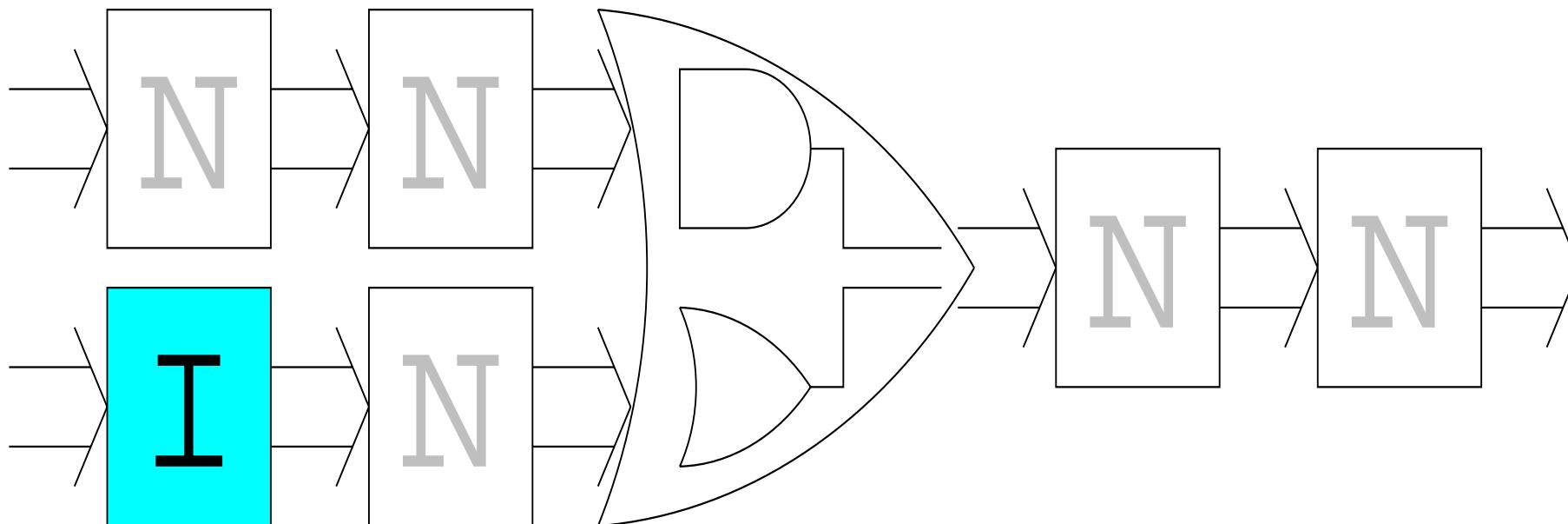


# Early Output Logic using Anti-Tokens

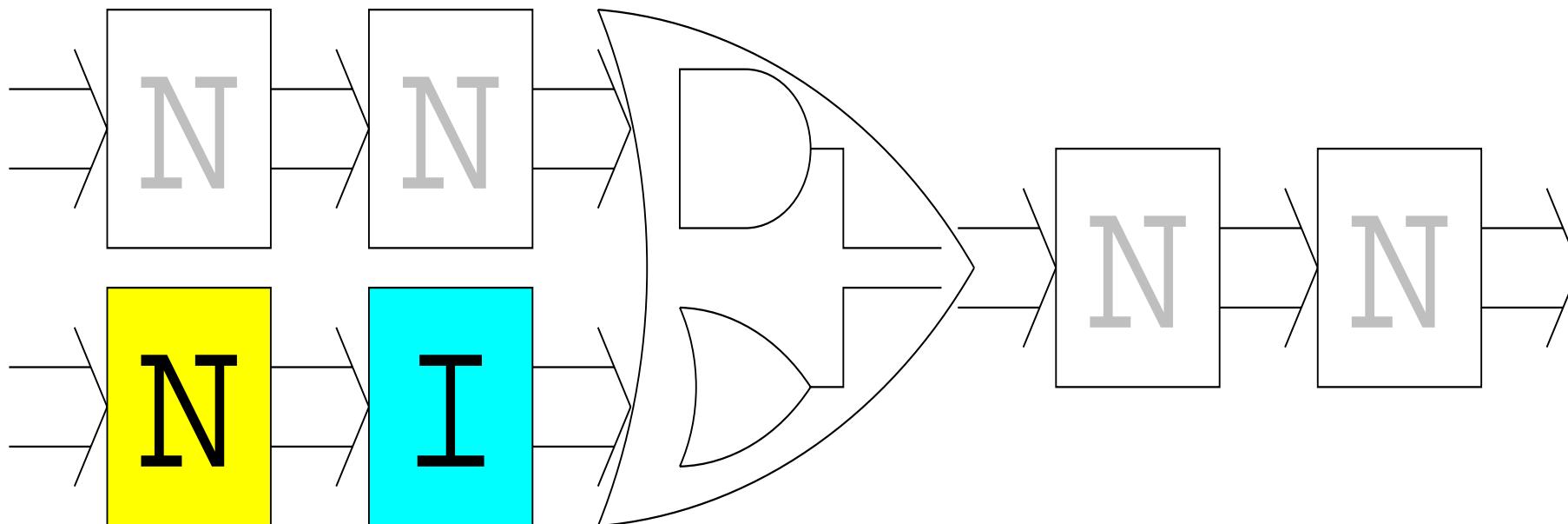

THE UNIVERSITY  
of MANCHESTER


# Early Output Logic using Anti-Tokens

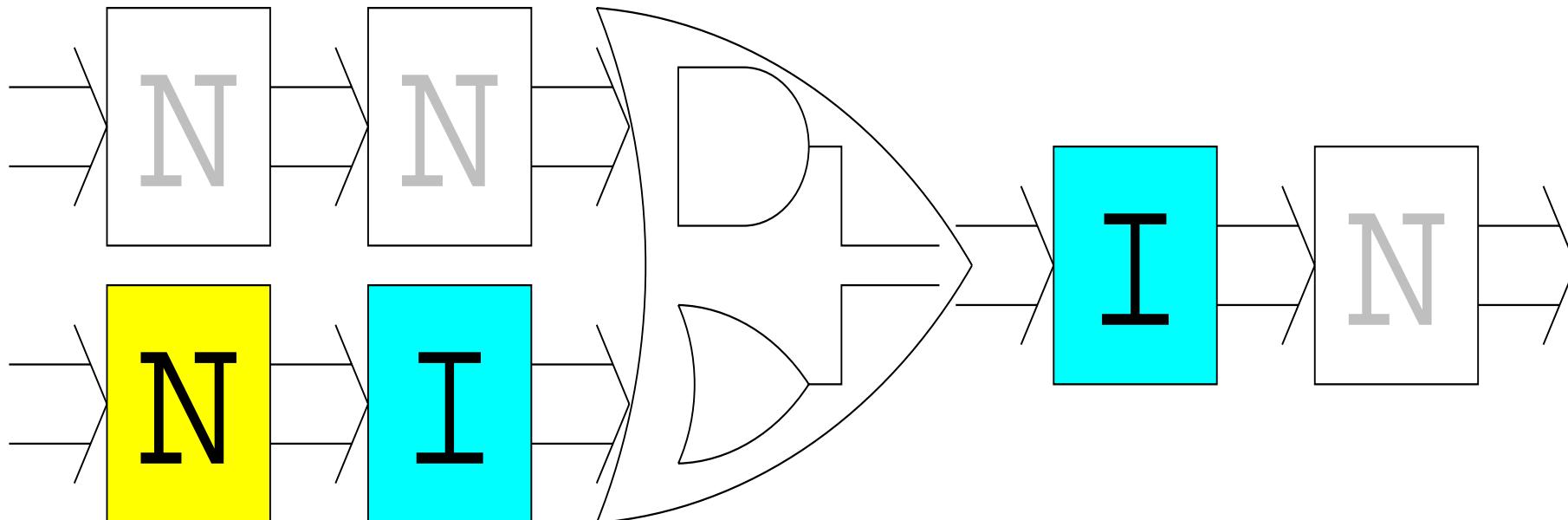

Data is sufficient to create a result  
Early output case



# Early Output Logic using Anti-Tokens

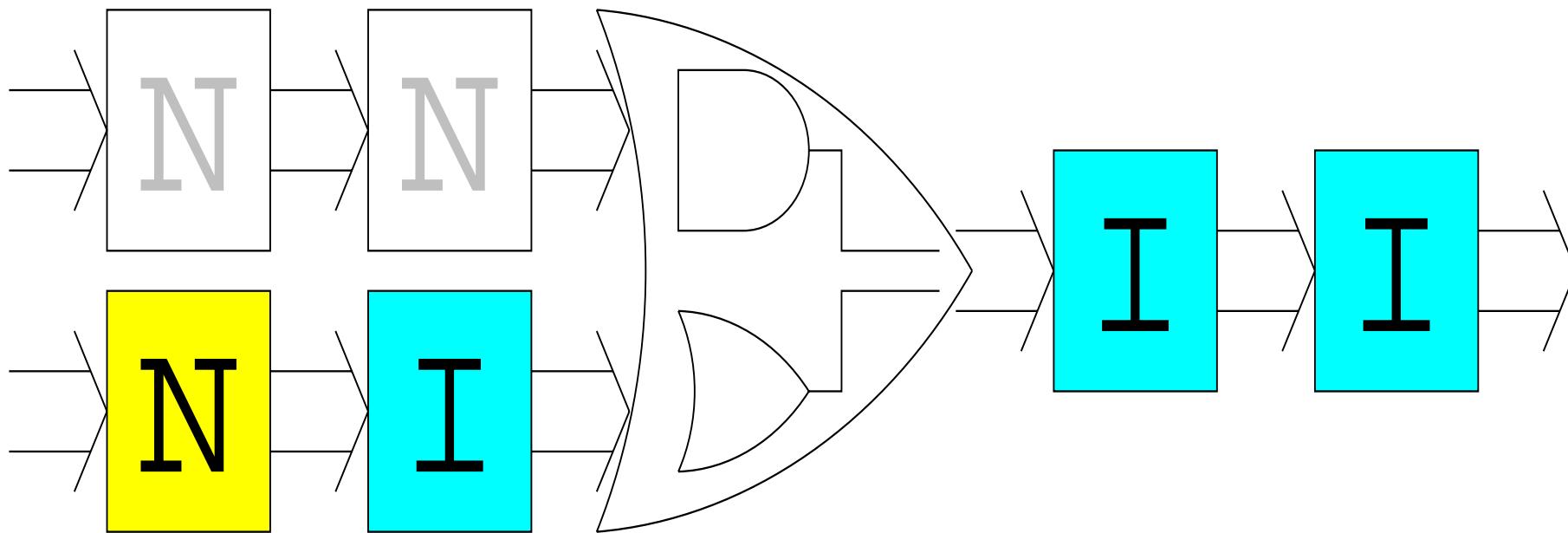

## Early output case


Safe

No acknowledgement until other input arrives

More early output cases



# Early Output Logic using Anti-Tokens

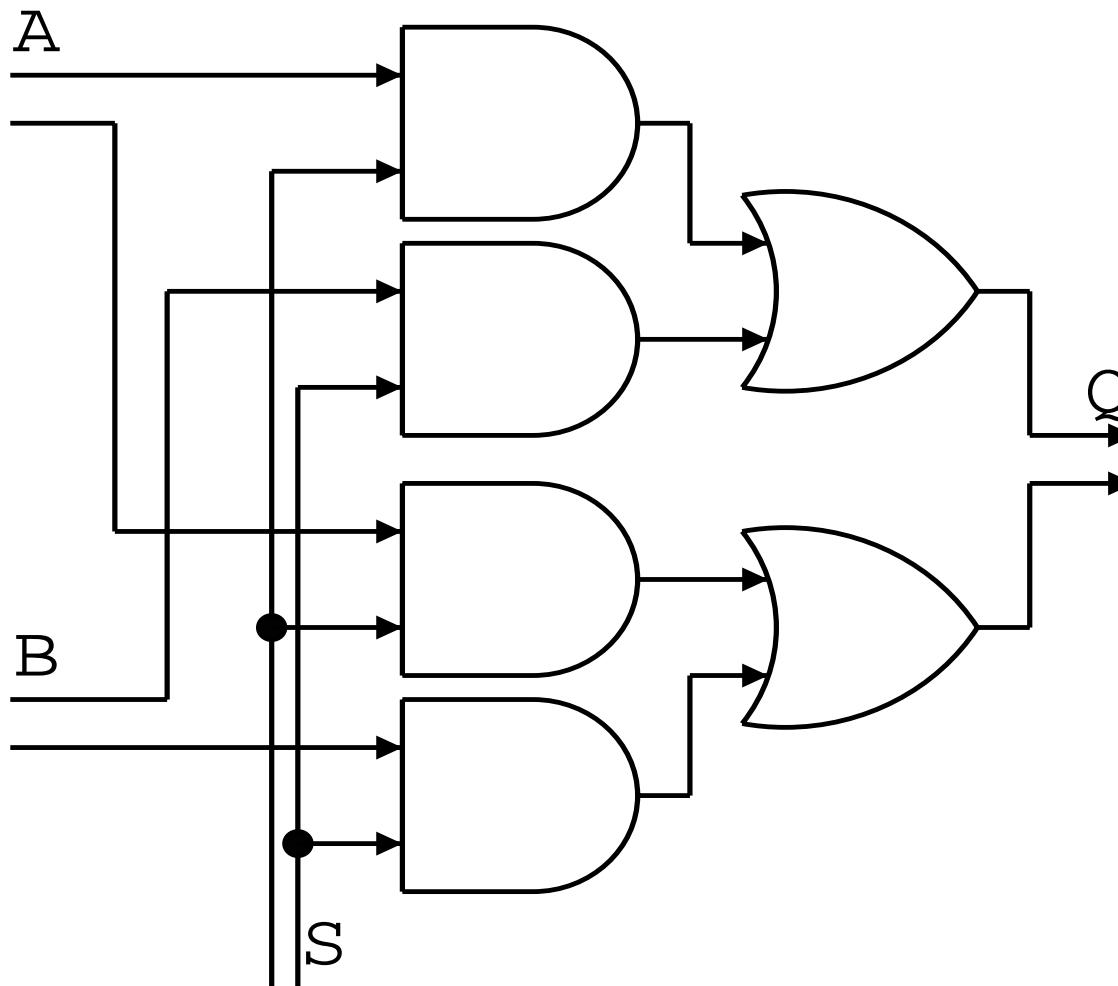


		S		
A	B	N	0	1
N	N	N	N	N
0	N	N	0*	N
1	N	N	1*	N
N	0	N	N	0*
0	0	N	0	0
1	0	N	1	0
N	1	N	N	1*
0	1	N	0	1
1	1	N	1	1

2:1 multiplexer design



# Early Output Logic using Anti-Tokens

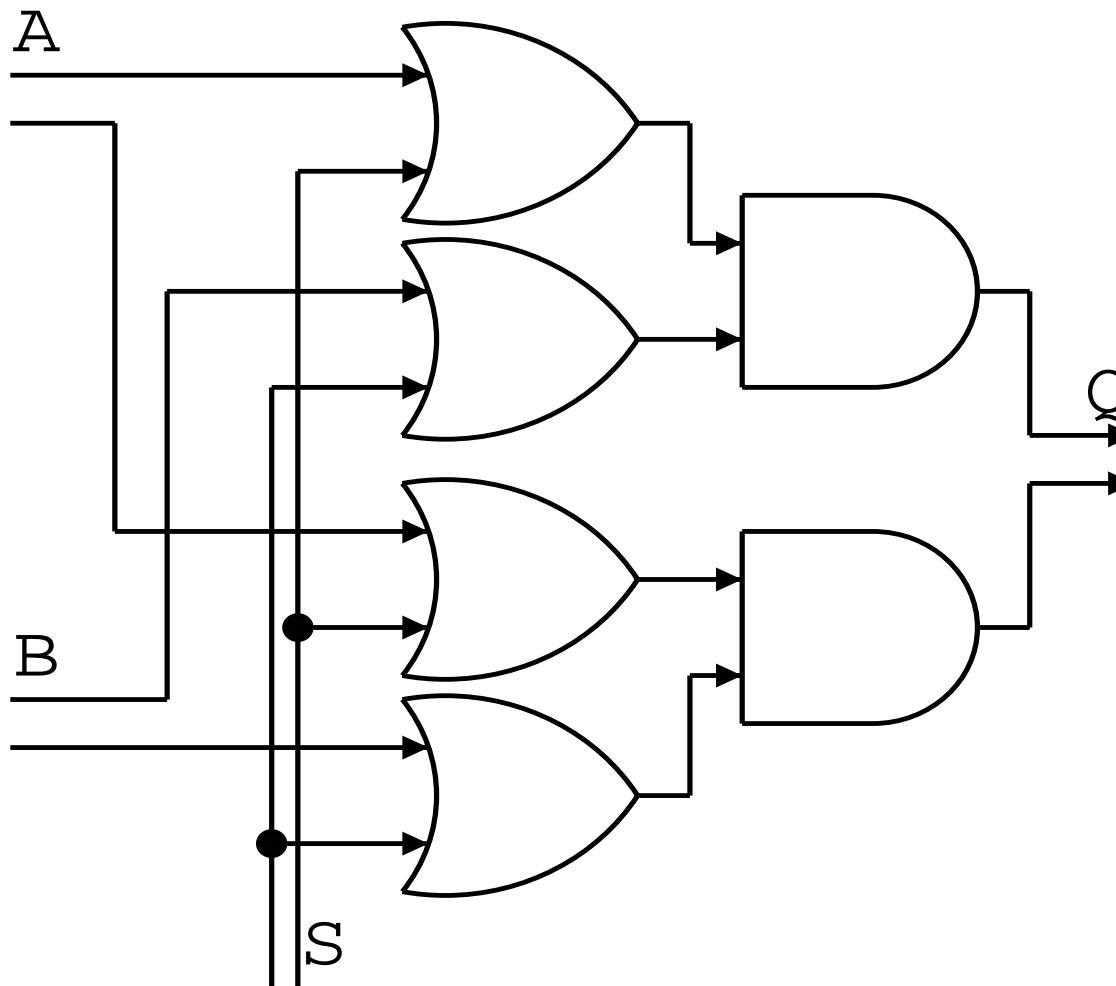


		S		
A	B	N	0	1
N	N	N	N	N
0	N	N	0*	N
1	N	N	1*	N
N	0	N	N	0*
0	0	0*	0	0
1	0	N	1	0
N	1	N	N	1*
0	1	N	0	1
1	1	1*	1	1

Alternative 2:1 multiplexer design  
Two more early output cases




# Early Output Logic using Anti-Tokens

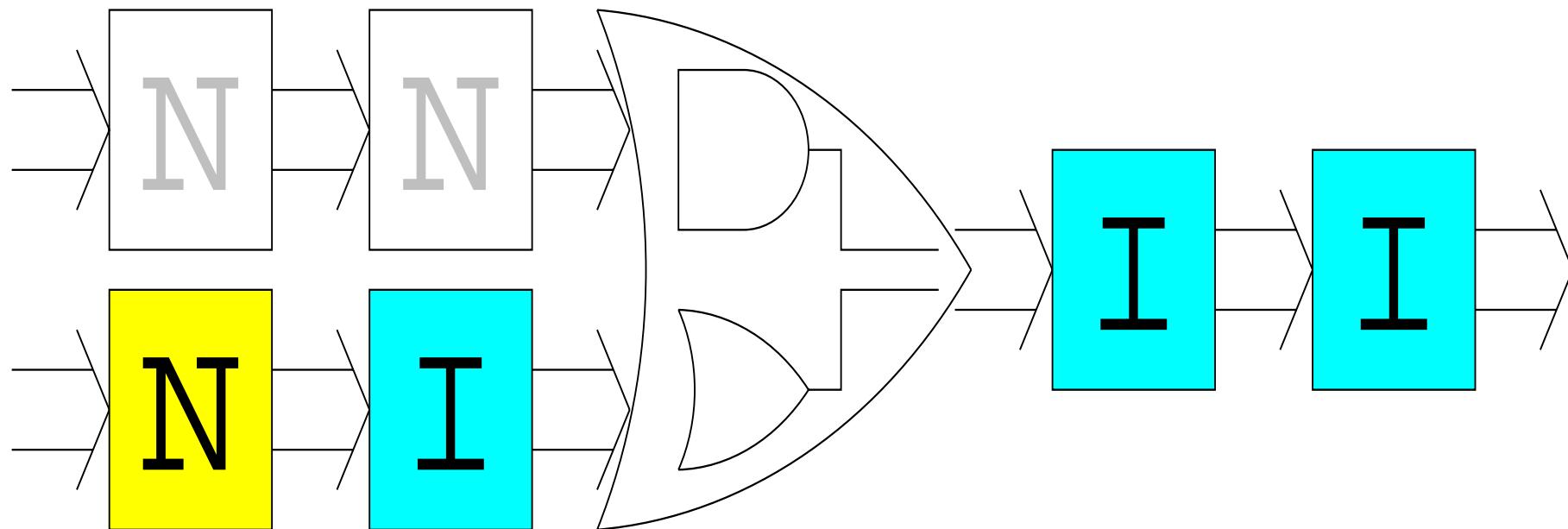

Stuck in data phase  
Semi-decoupled latch




## Early Output Logic using Anti-Tokens

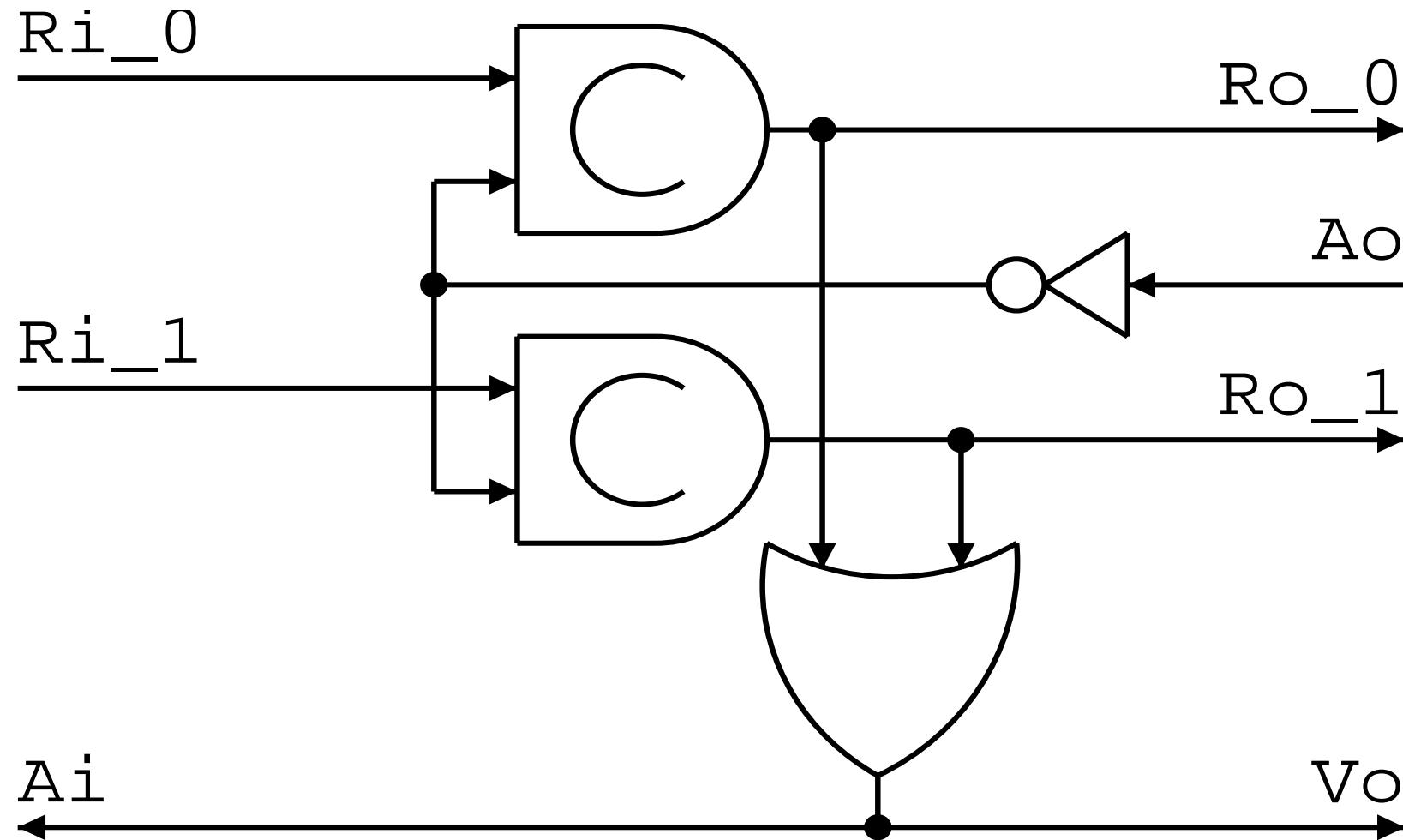

Standard dual-rail latch  
Ro- transition requires Ri-




# Early Output Logic using Anti-Tokens

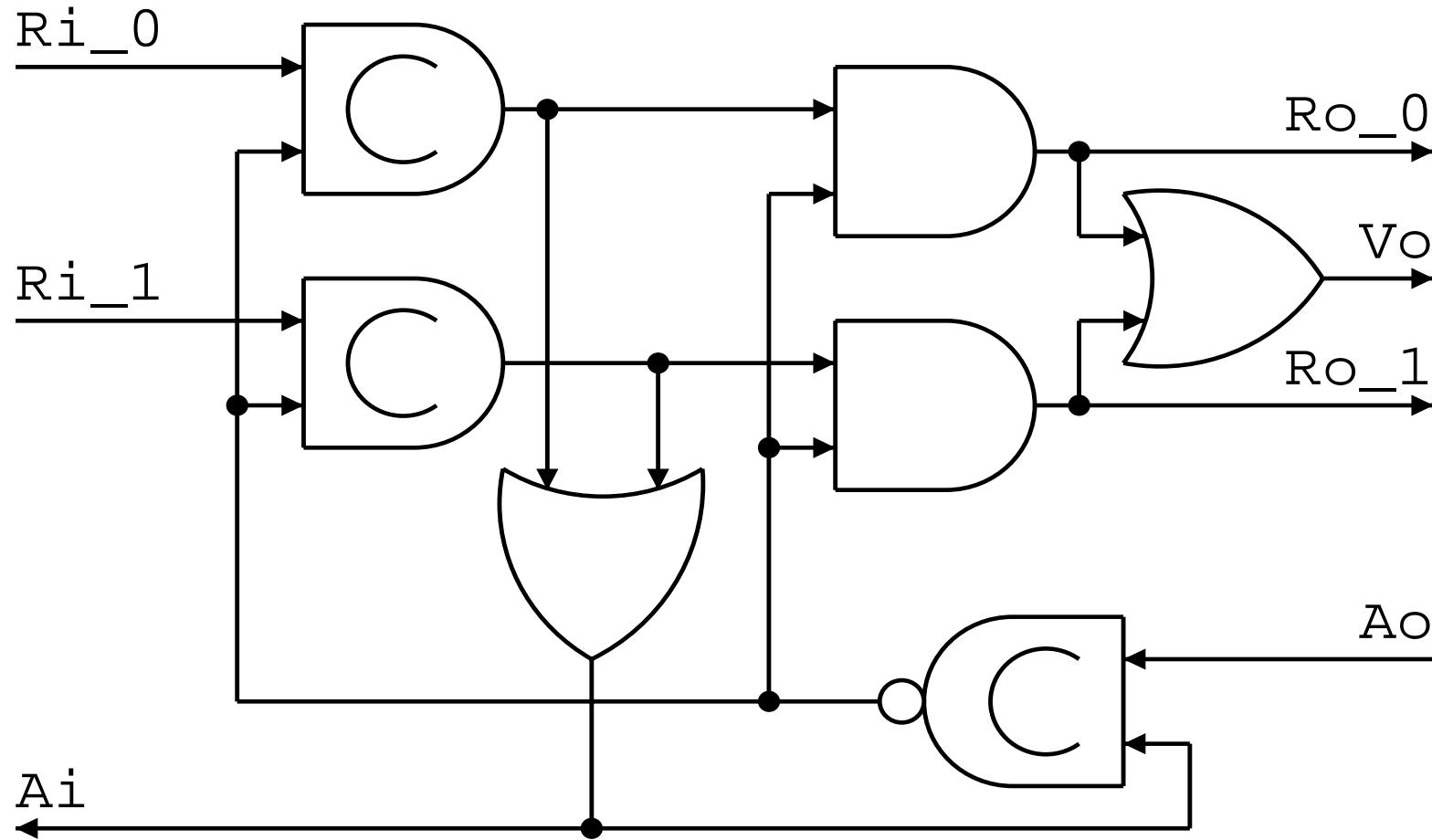

Standard semi-decoupled latch  
Ro is forced low  
Expensive




# Early Output Logic using Anti-Tokens

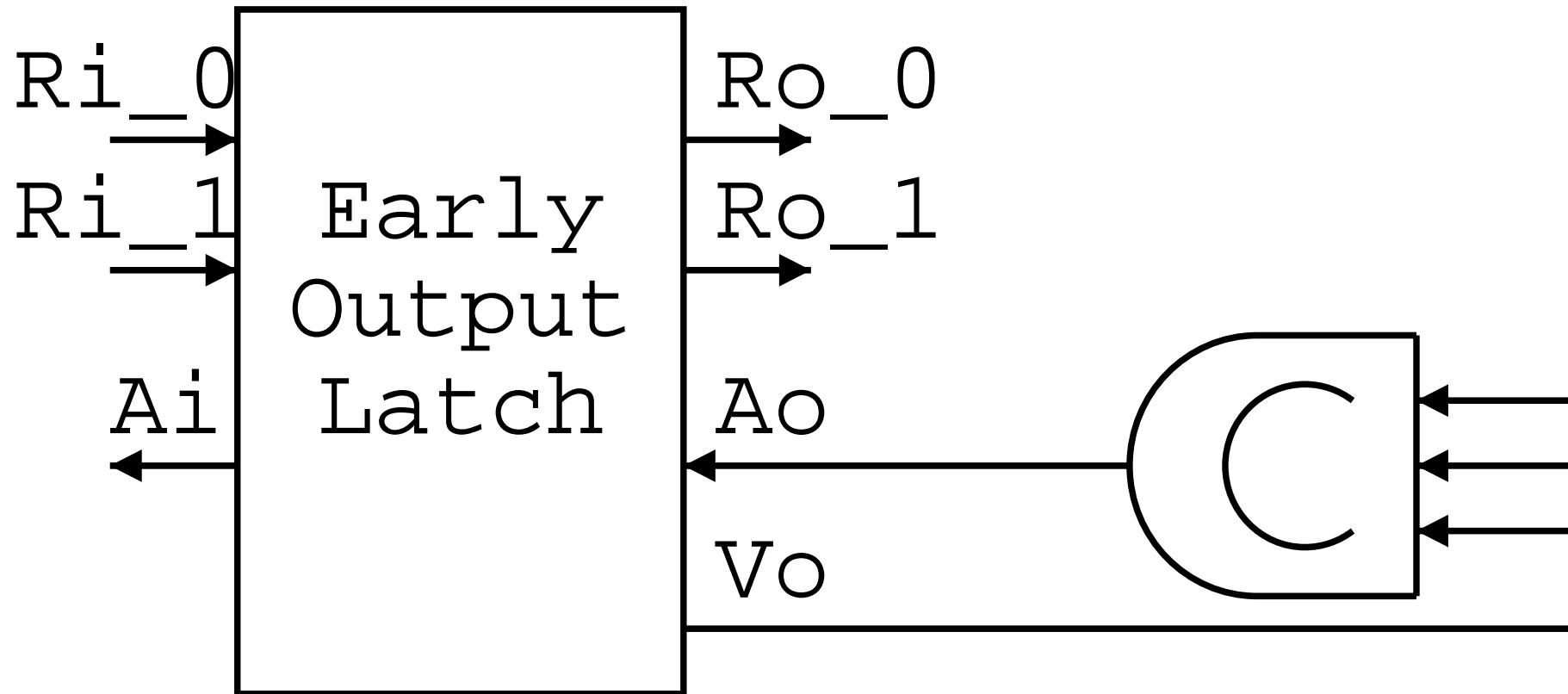

Validity to acknowledge connection




# Early Output Logic using Anti-Tokens

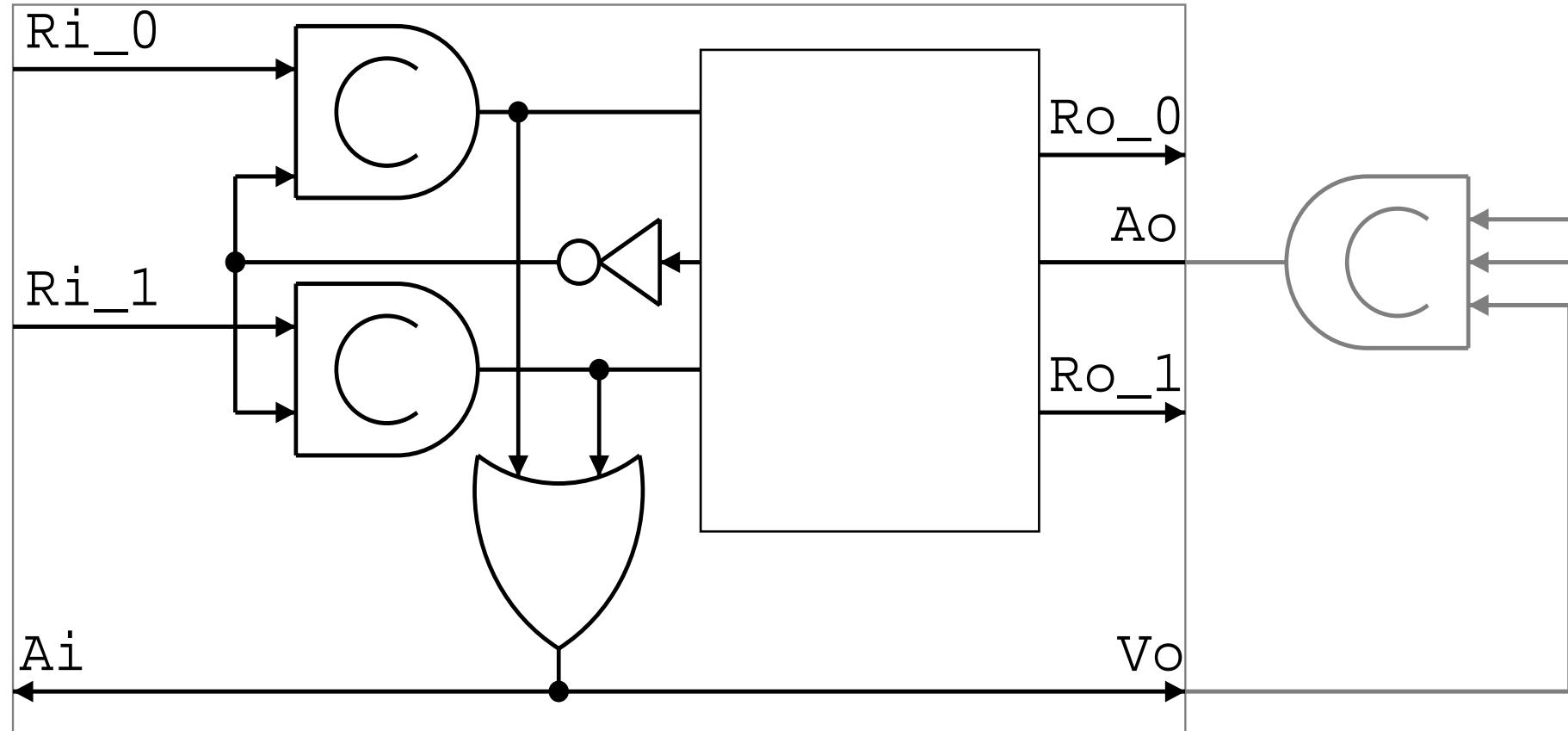

Early output semi-decoupled latch




# Early Output Logic using Anti-Tokens

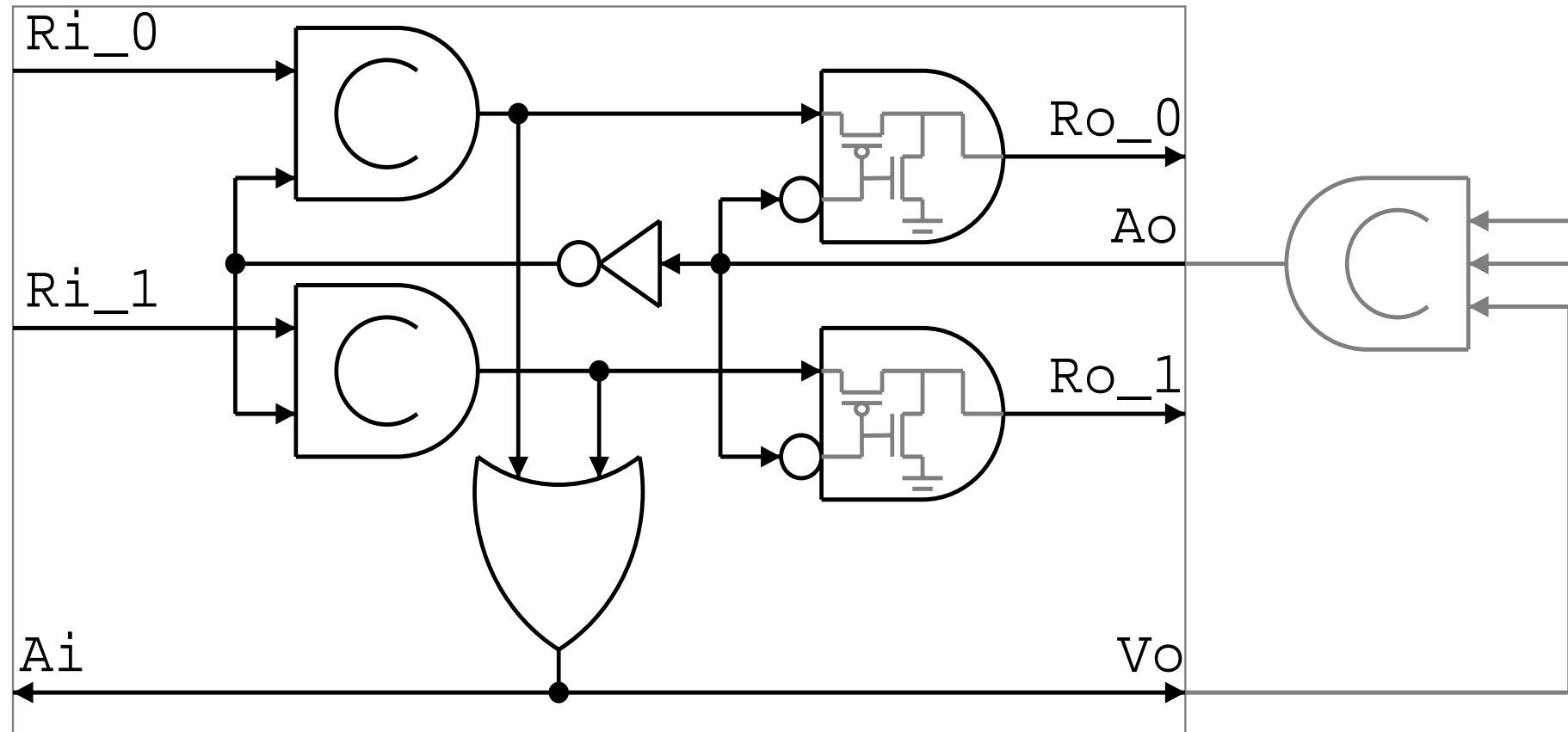


Early output semi-decoupled latch




# Early Output Logic using Anti-Tokens

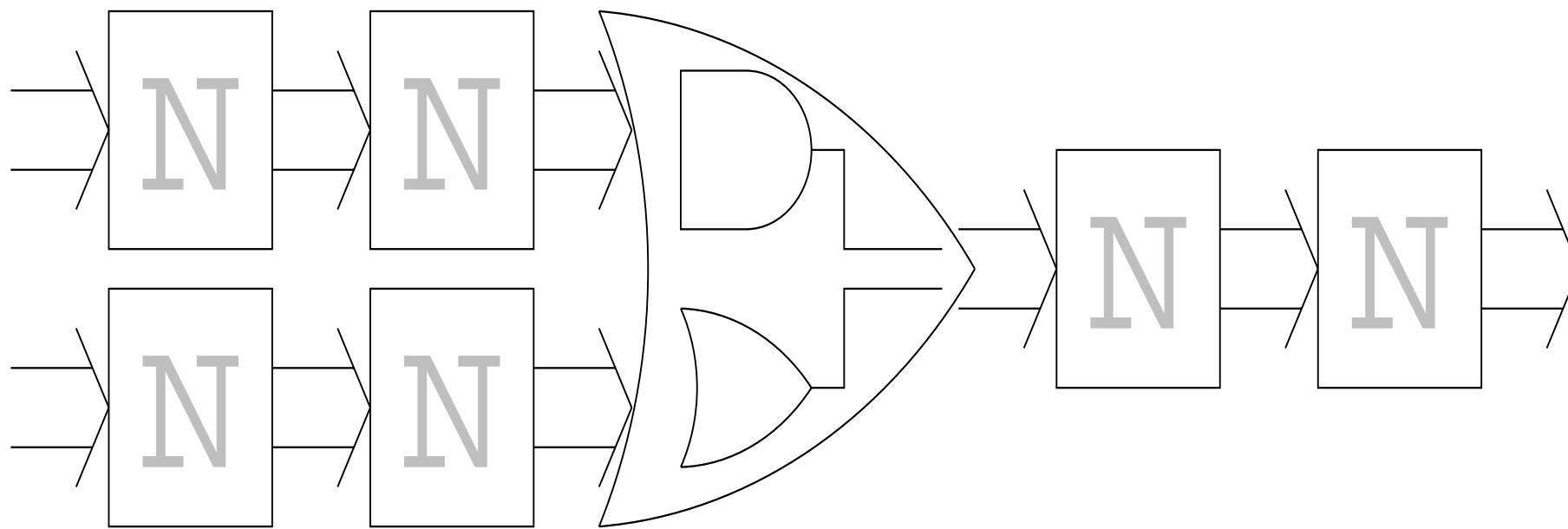


# Early Output Logic using Anti-Tokens

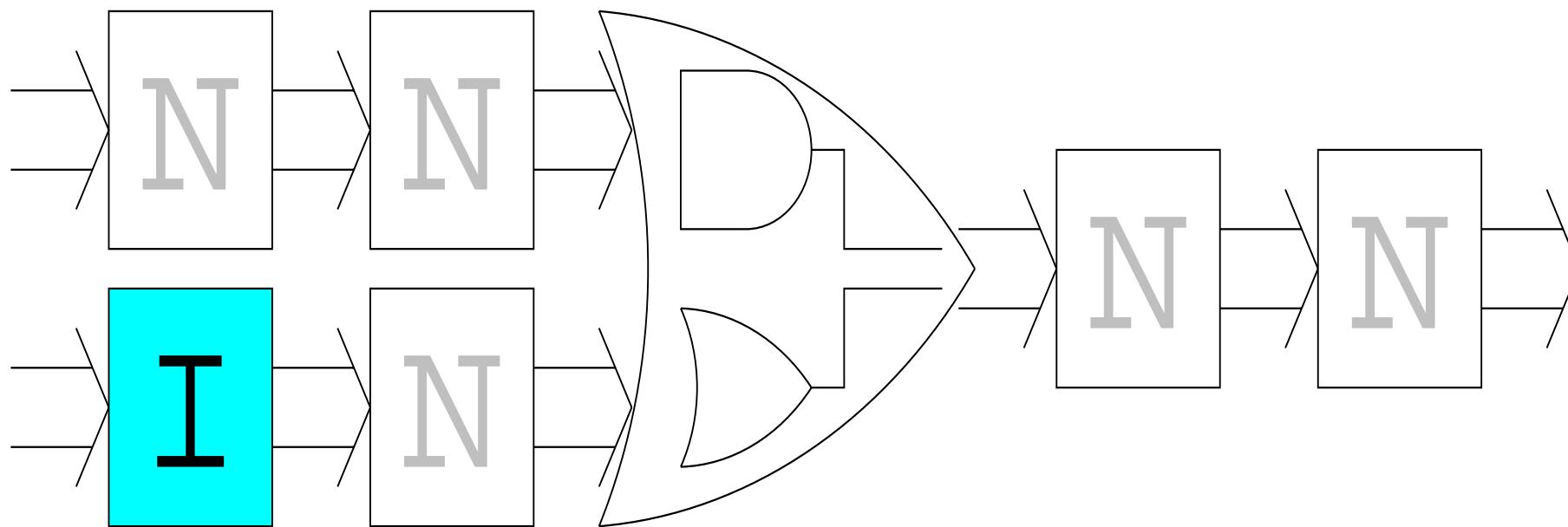


# Early Output Logic using Anti-Tokens

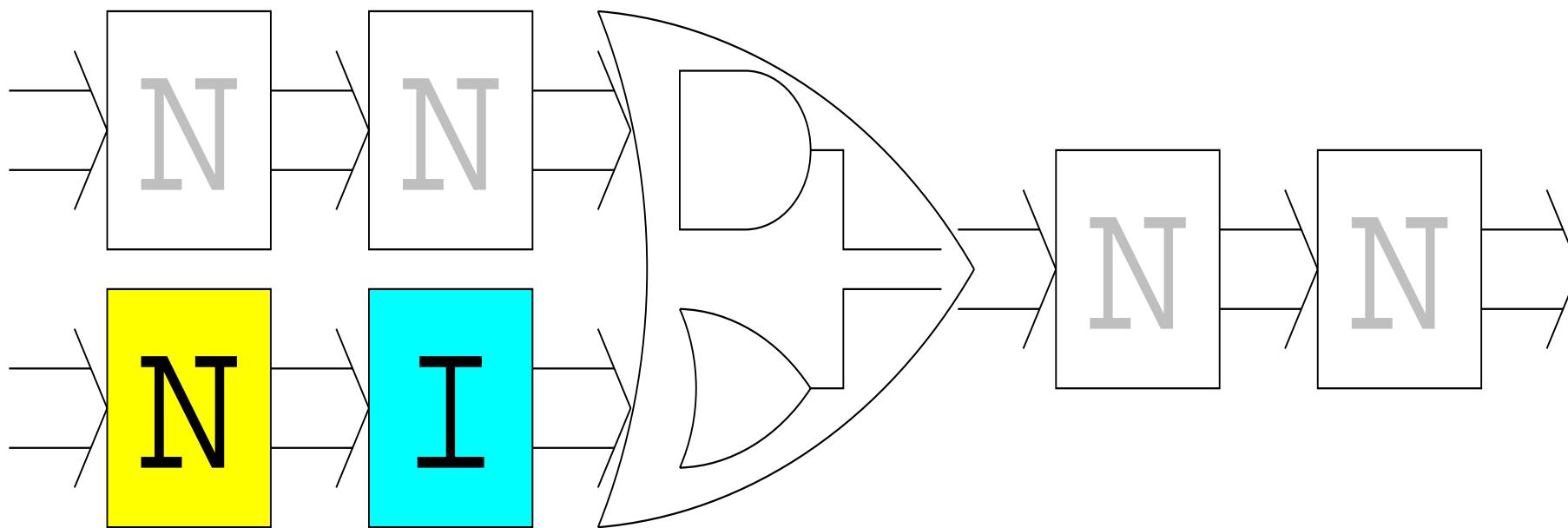


# Early Output Logic using Anti-Tokens

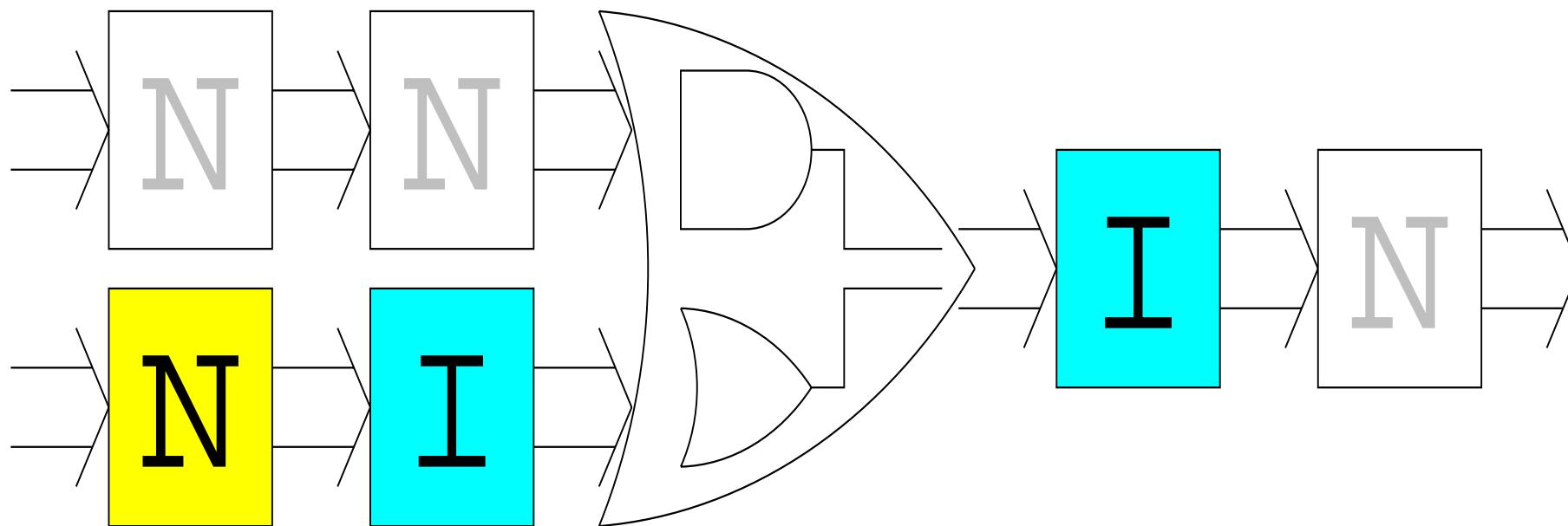

# Early Output Logic using Anti-Tokens

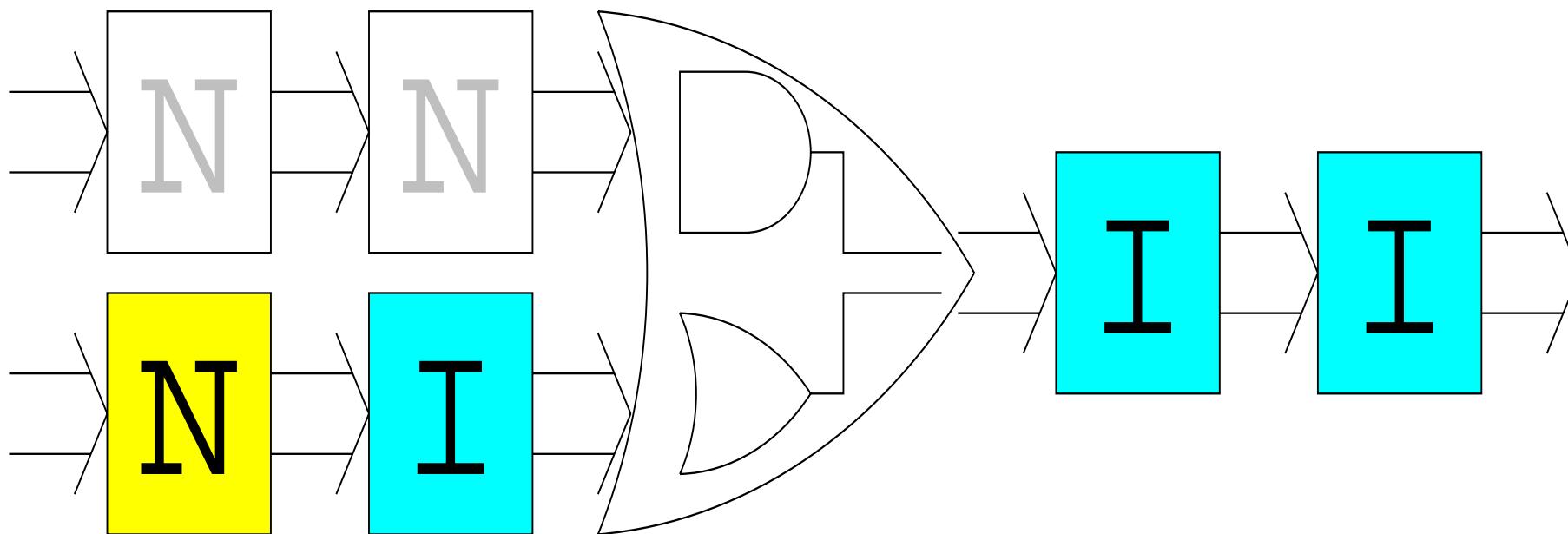


# Early Output Logic using Anti-Tokens

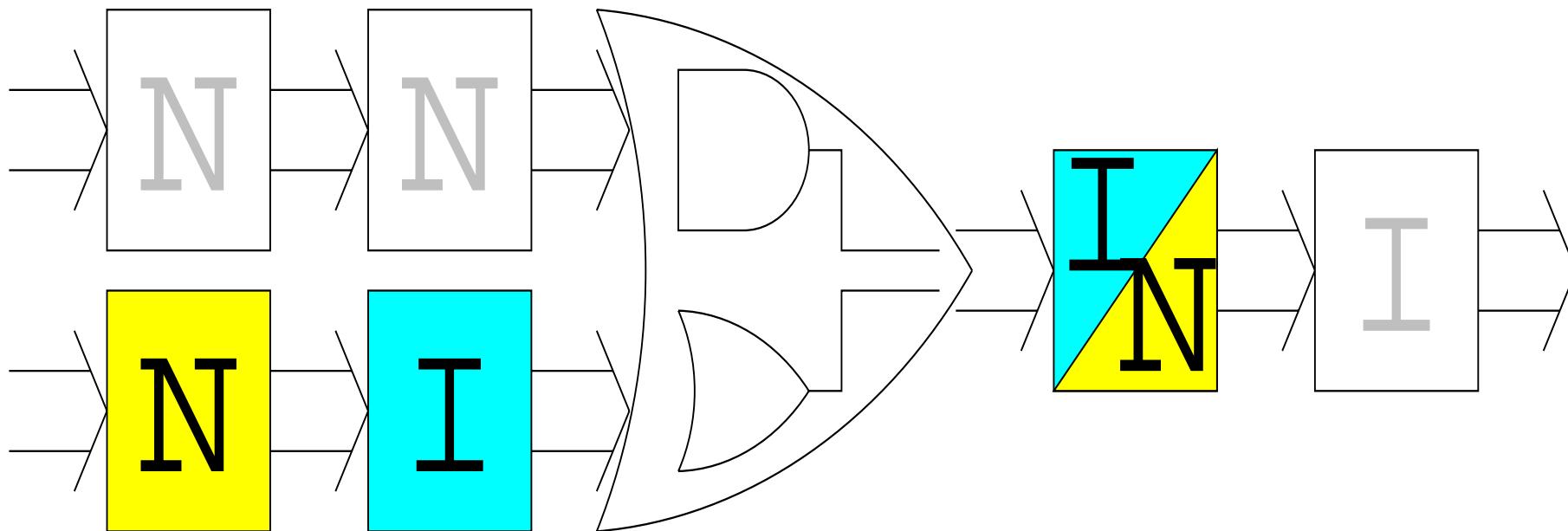


Semi-decoupled latch outputs a NULL



# Early Output Logic using Anti-Tokens

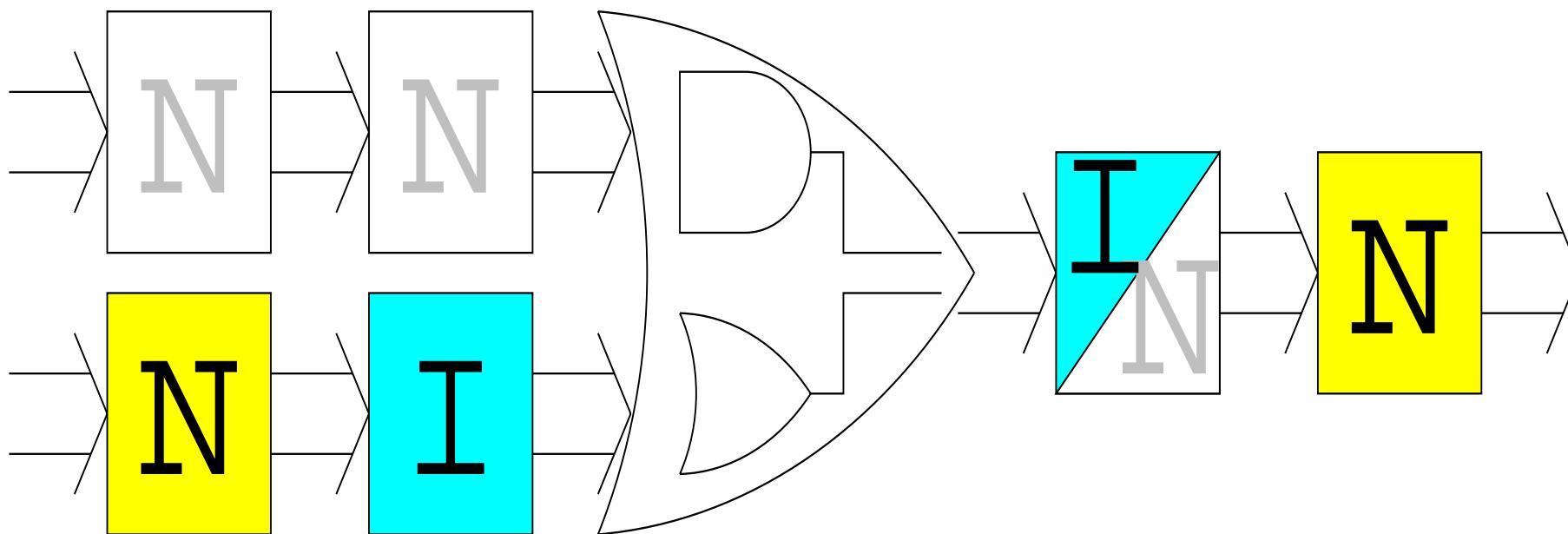

# Early Output Logic using Anti-Tokens

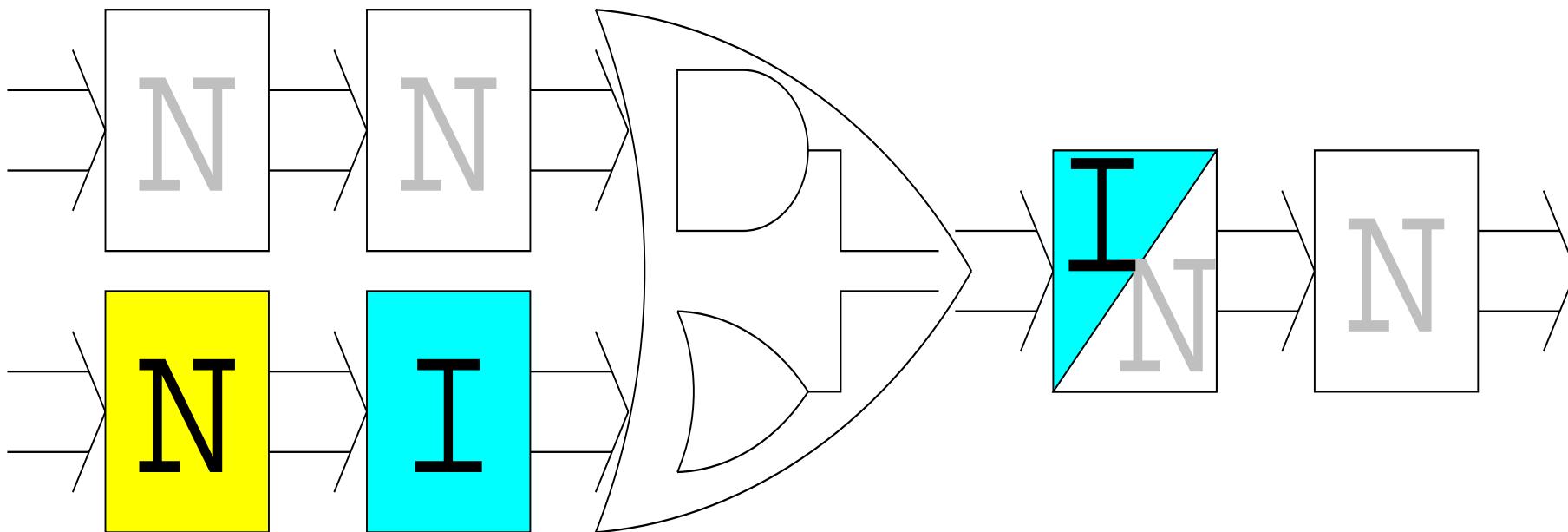

Later stages free to continue but OR gate is stuck  
Tell top pipeline to throw away next token

## Anti-Token Latches

Assert validity early


Receive acknowledge early

Hold an anti-token

Pass an anti-token backwards




# Early Output Logic using Anti-Tokens

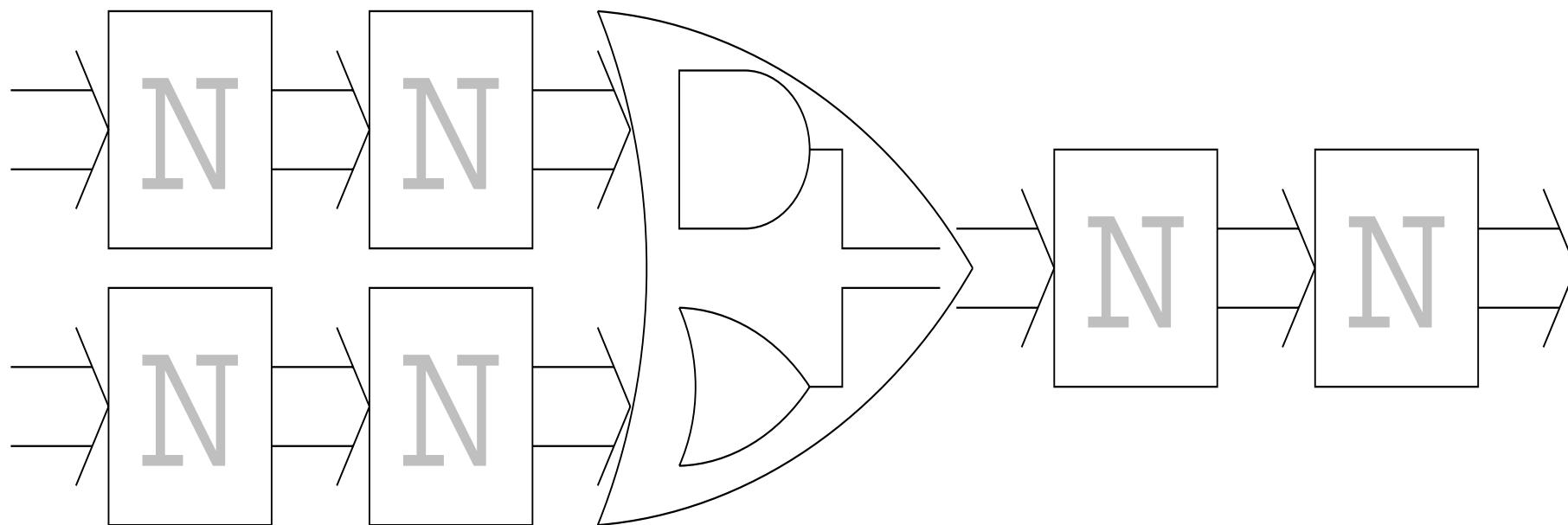


THE UNIVERSITY  
of MANCHESTER


# Early Output Logic using Anti-Tokens

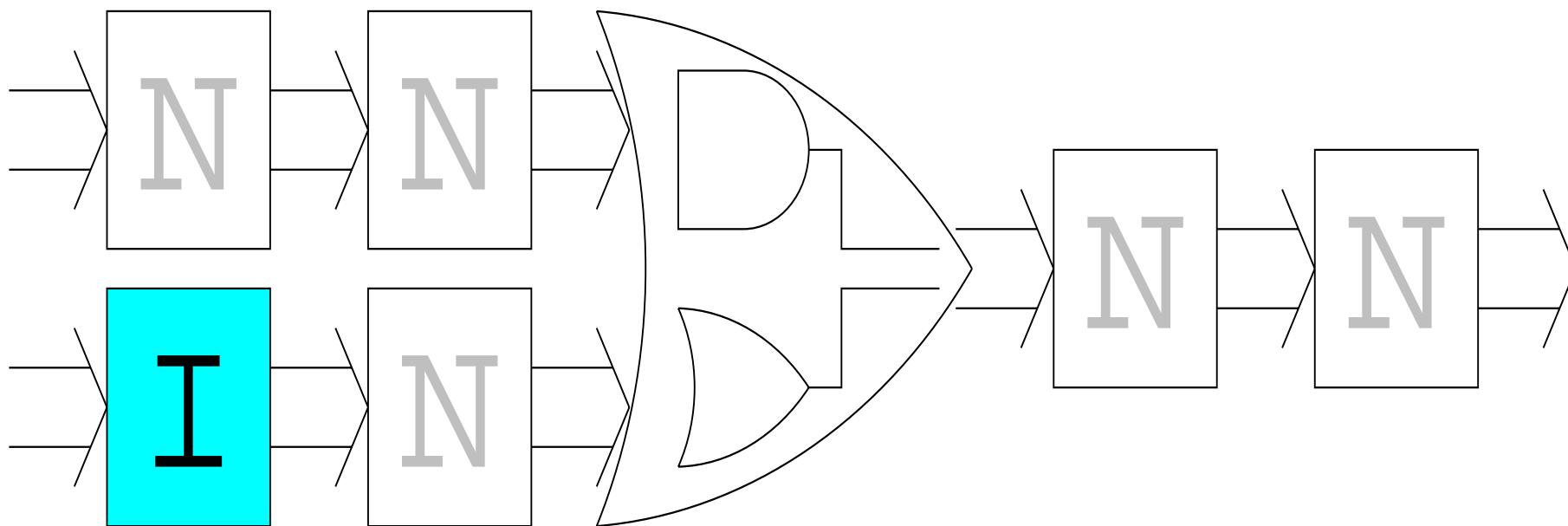

# Early Output Logic using Anti-Tokens

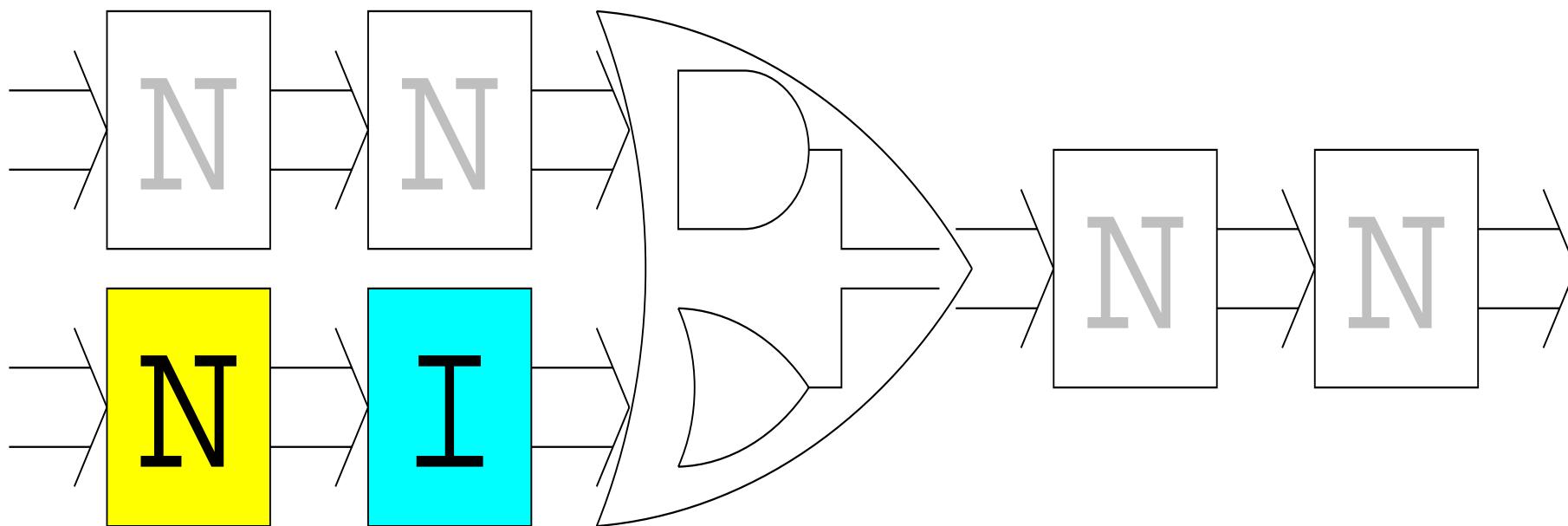


# Early Output Logic using Anti-Tokens

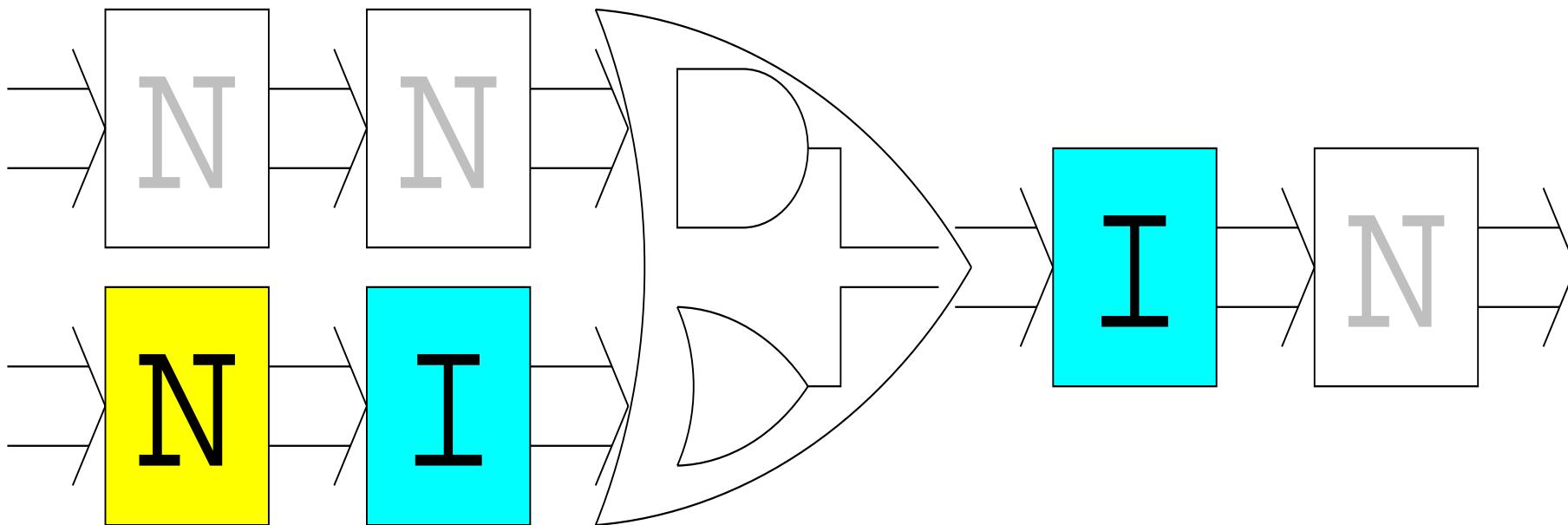

Data generated so latch acknowledges  
Top latch asserts validity early




# Early Output Logic using Anti-Tokens

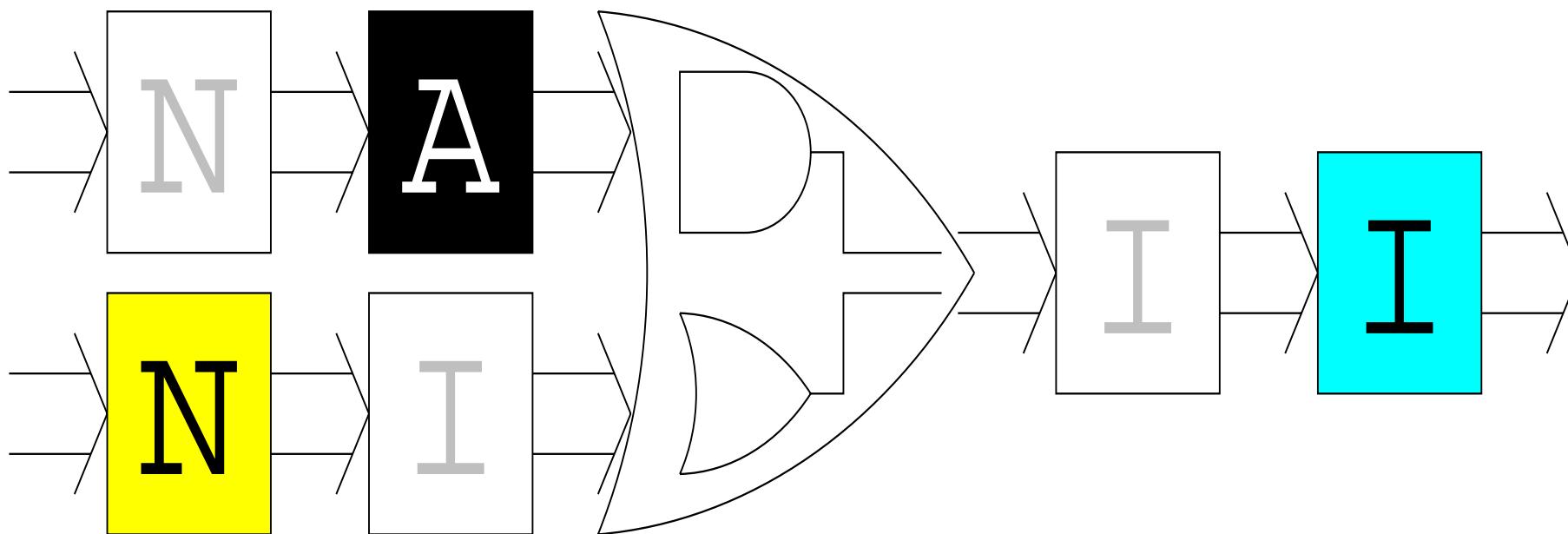


Top latch receives an anti-token




# Early Output Logic using Anti-Tokens

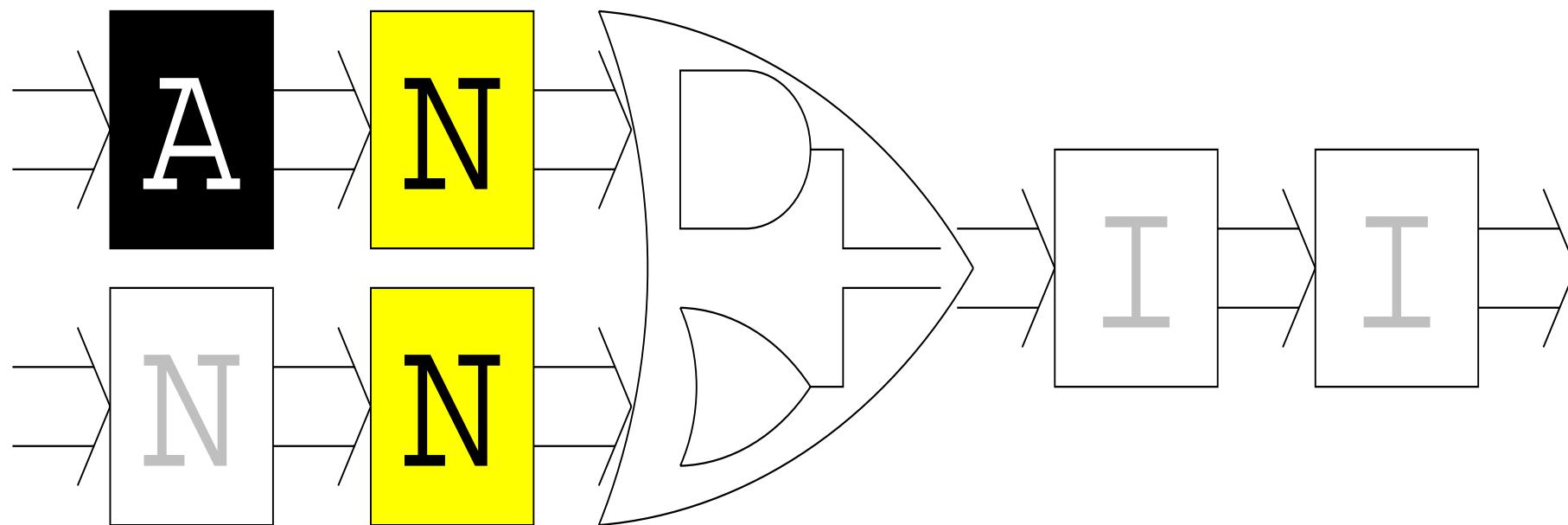

# Early Output Logic using Anti-Tokens

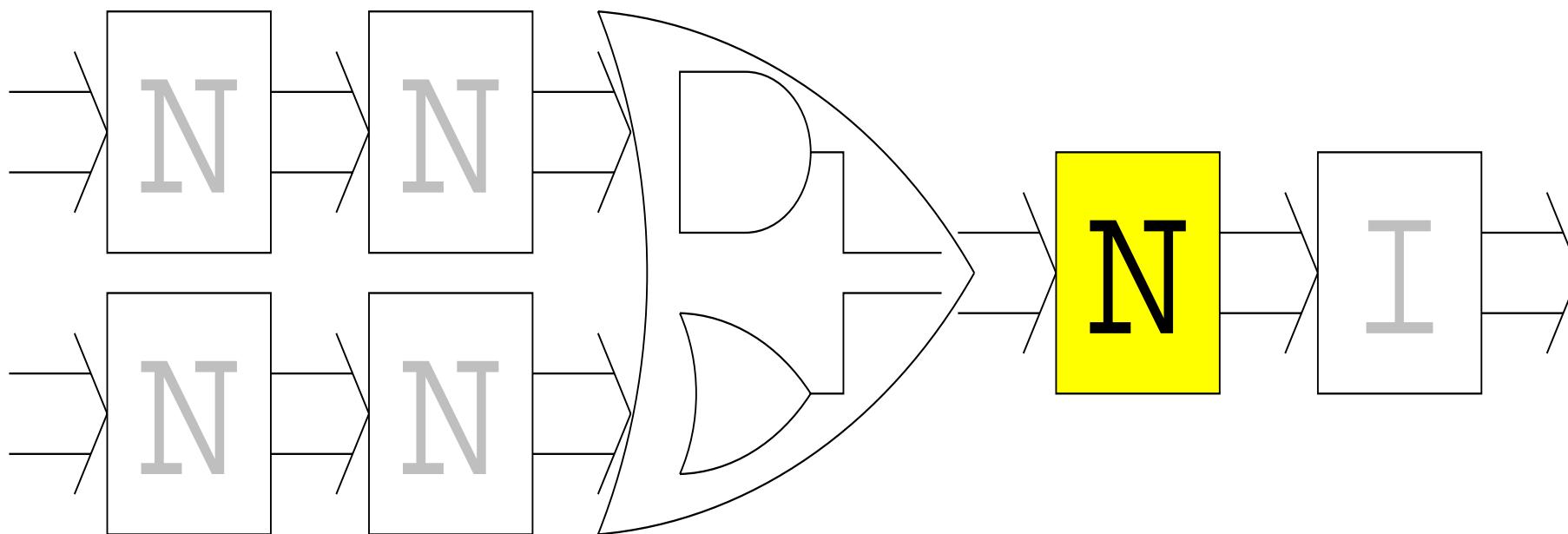


# Early Output Logic using Anti-Tokens

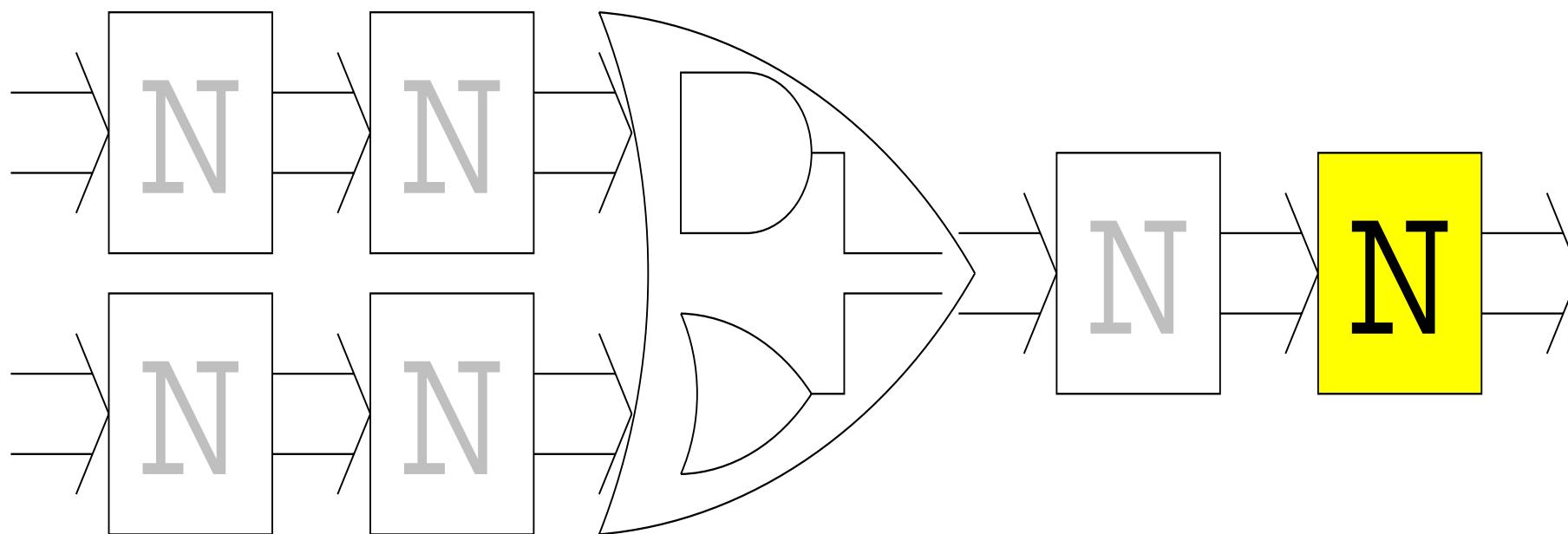

THE UNIVERSITY  
of MANCHESTER


# Early Output Logic using Anti-Tokens

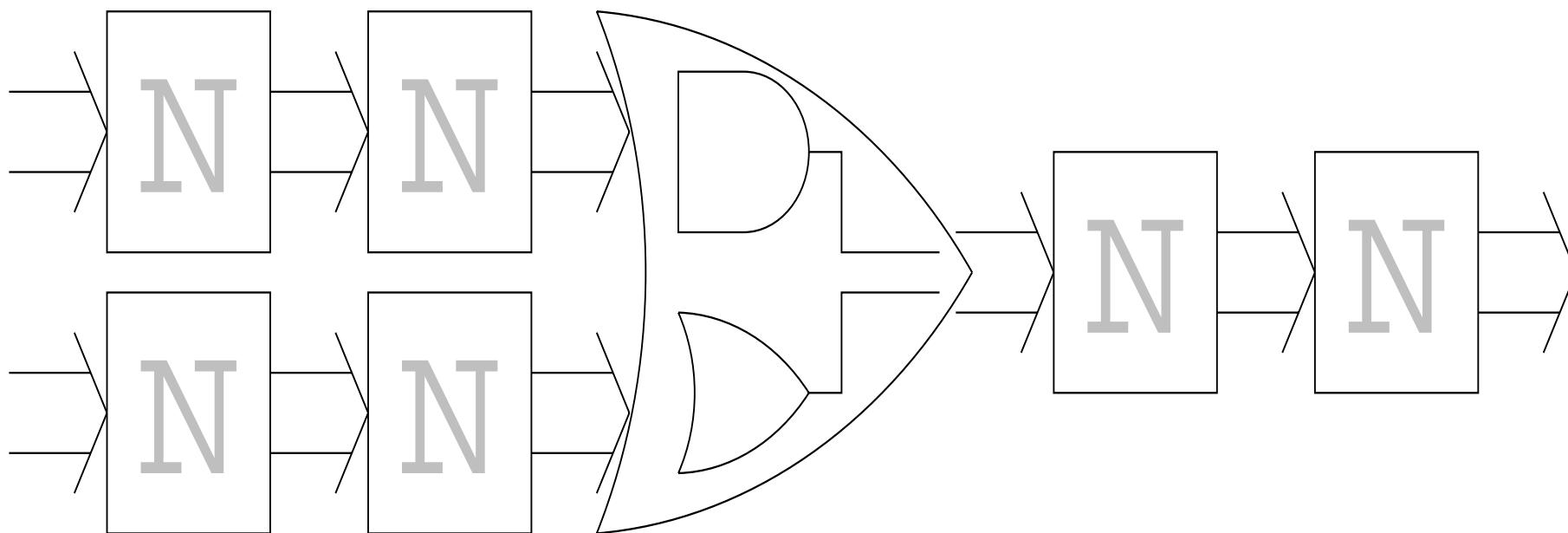


Ready to accept next set of inputs




# Early Output Logic using Anti-Tokens

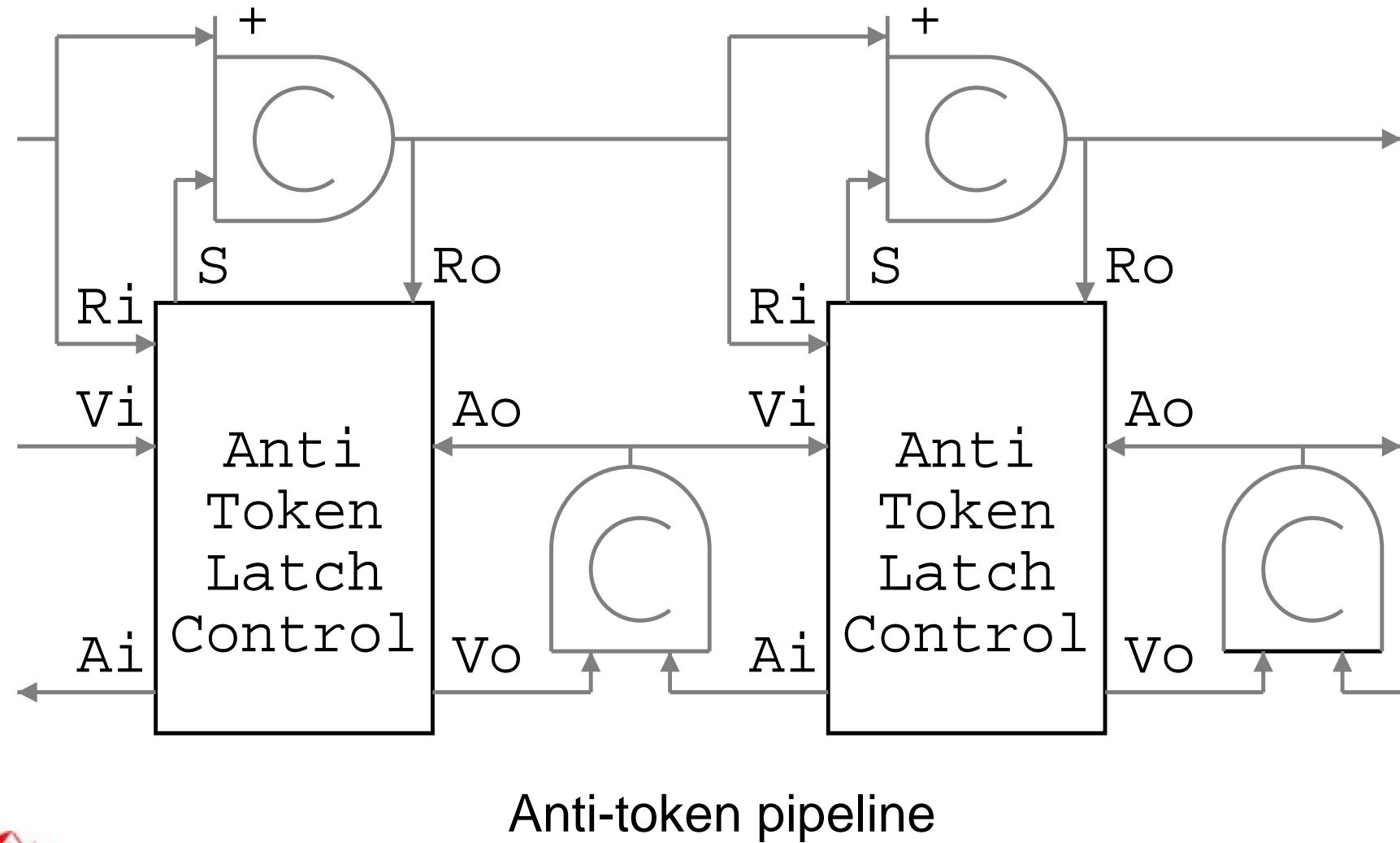

# Early Output Logic using Anti-Tokens

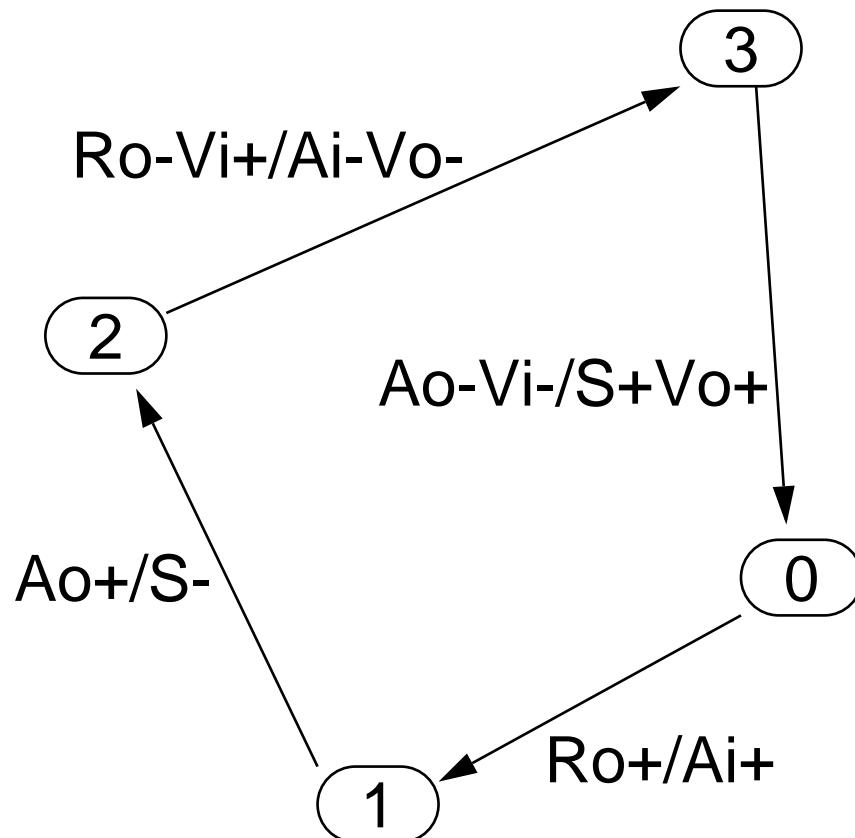


**MINIMALIST**  
Inputs/Outputs

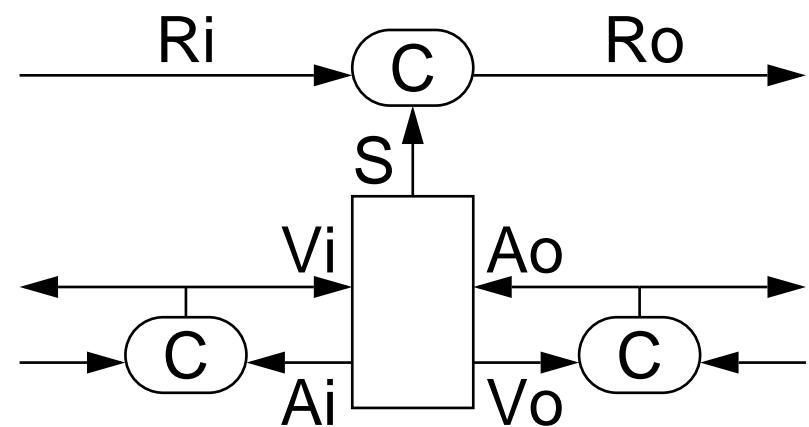


THE UNIVERSITY  
of MANCHESTER

# Early Output Logic using Anti-Tokens


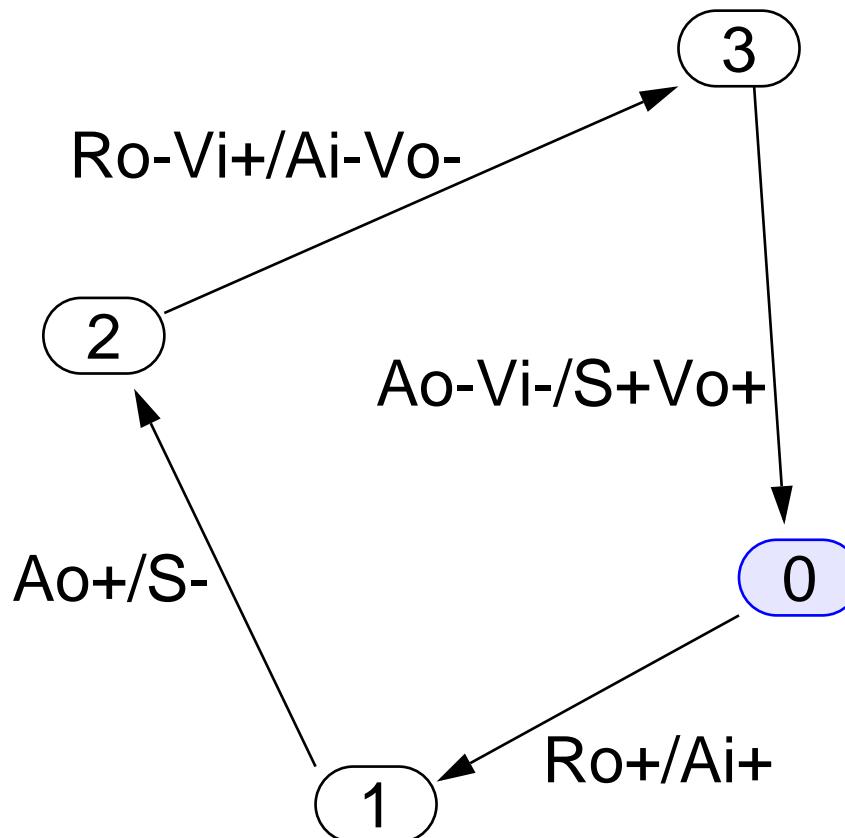


Initial state:0  
 $S, Vo = 1$   
 $Ri, Ro, Vi, Ai, Ao = 0$



Note: Both C-elements primed to fire

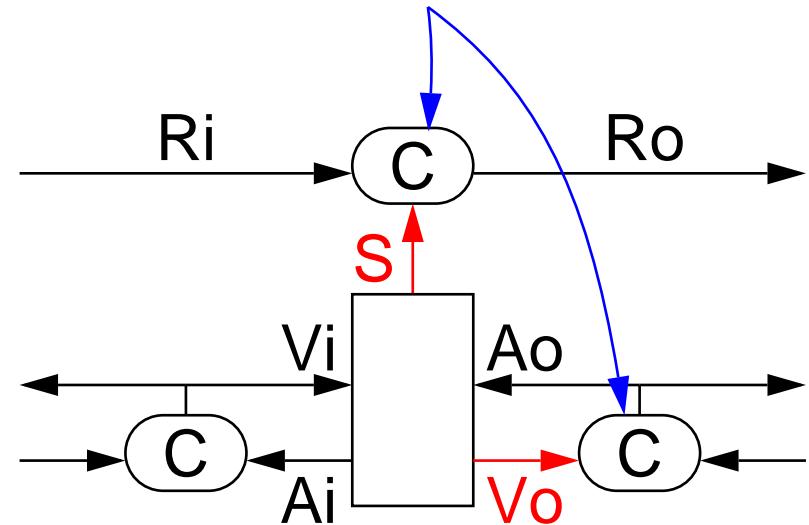

# Early Output Logic using Anti-Tokens

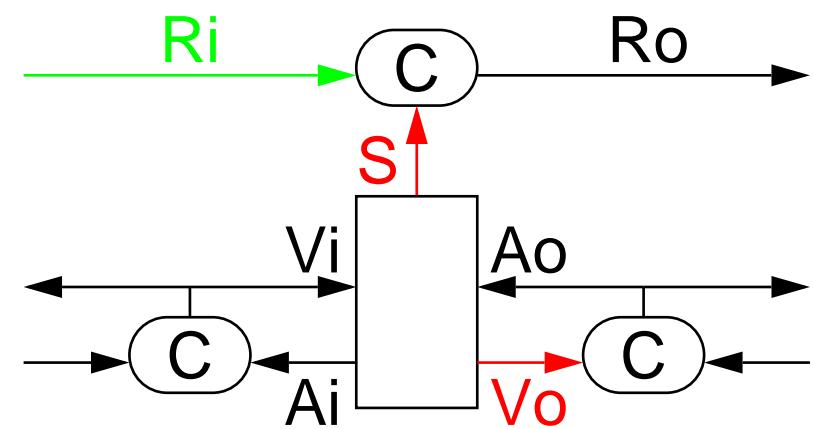
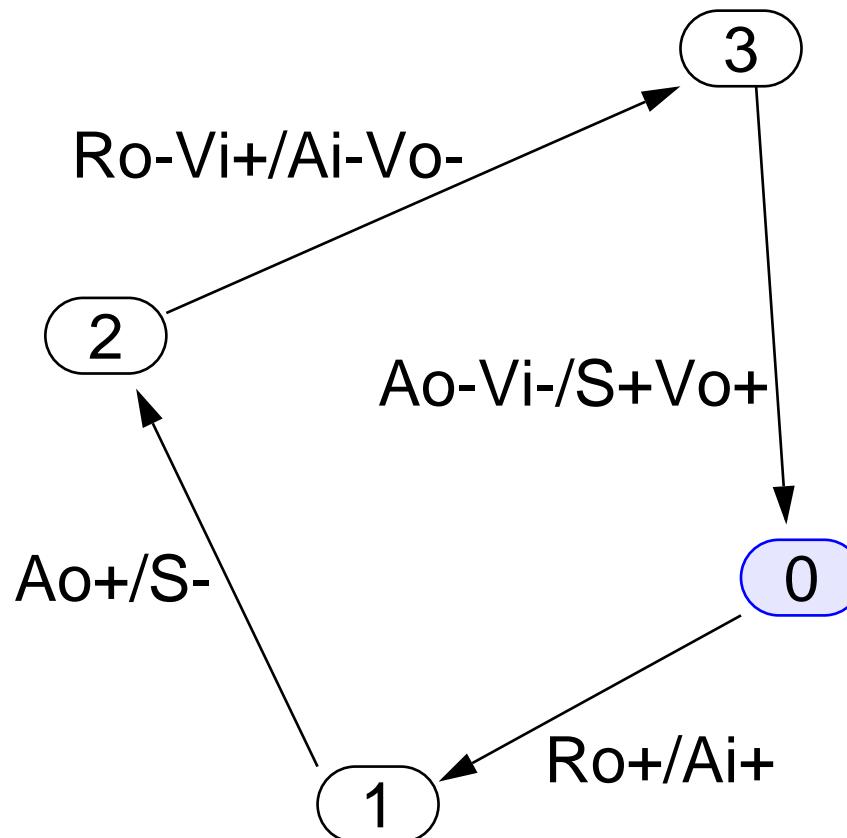


# Early Output Logic using Anti-Tokens

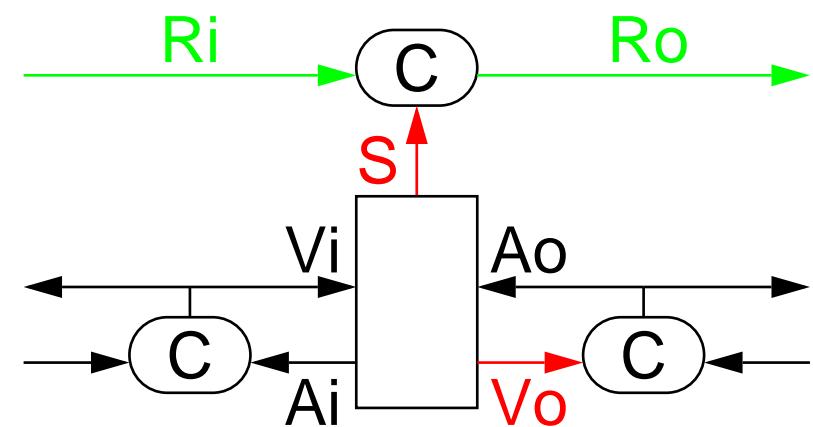
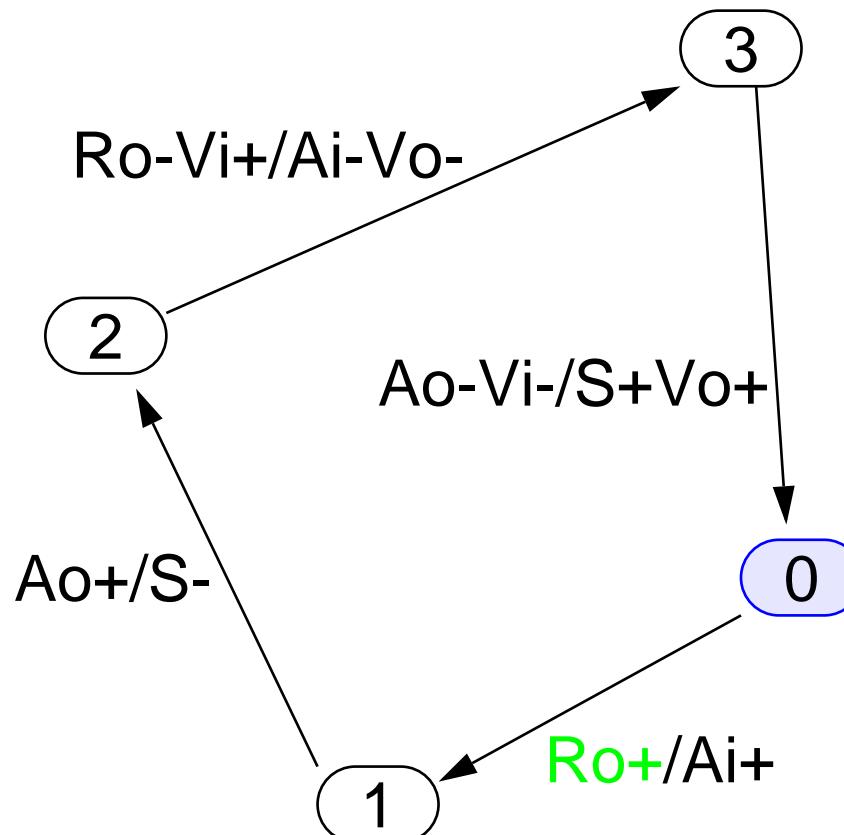


THE UNIVERSITY  
of MANCHESTER

# Early Output Logic using Anti-Tokens

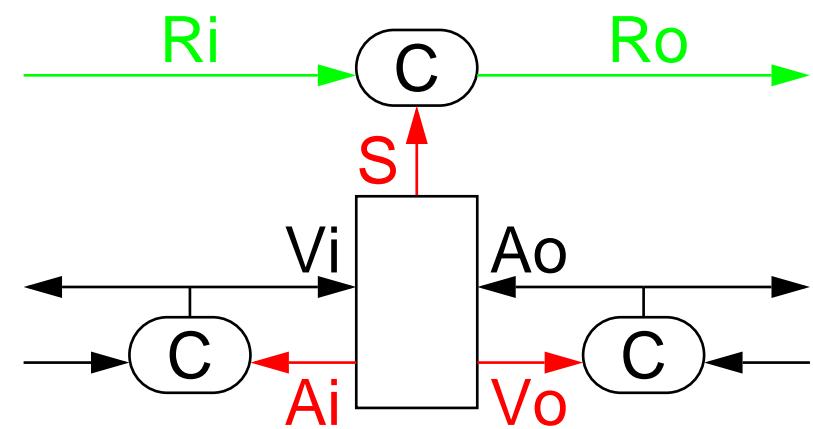
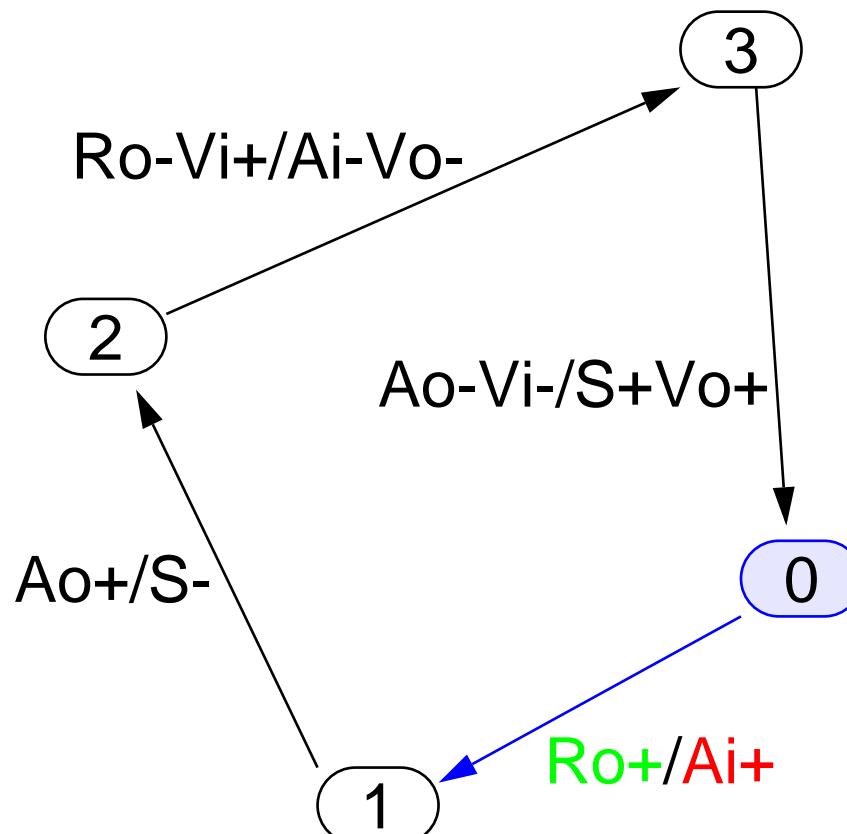


# Early Output Logic using Anti-Tokens

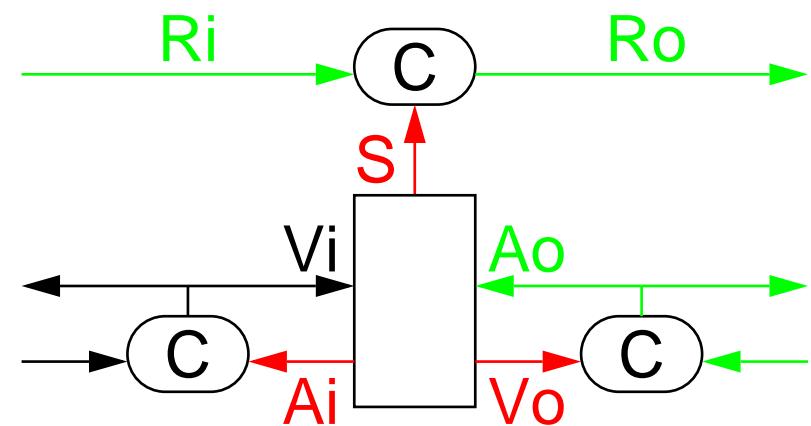
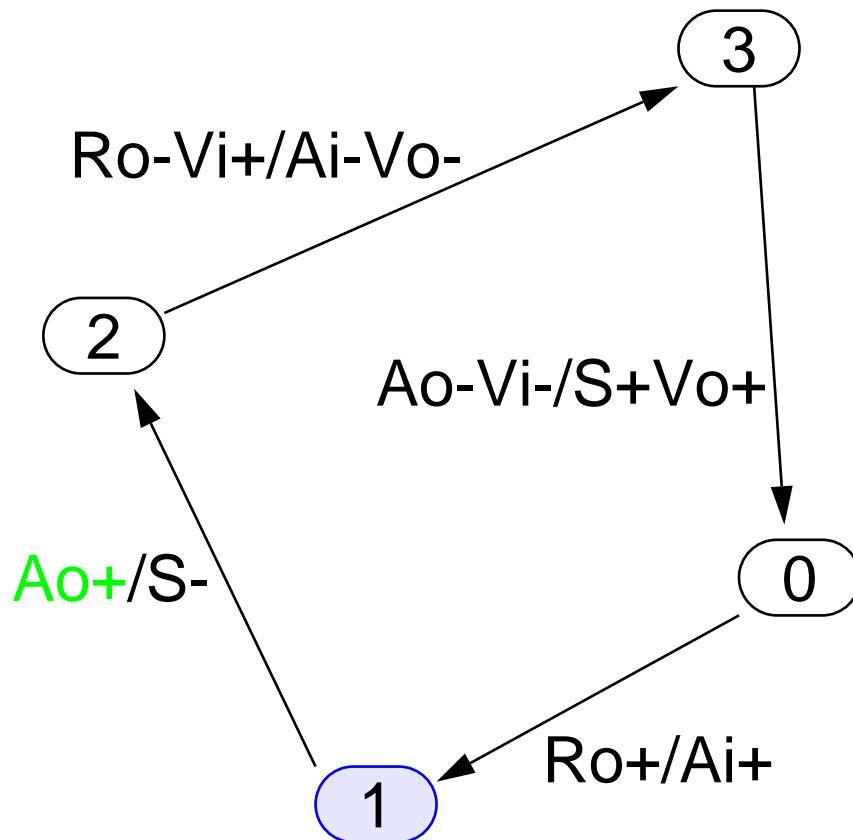


THE UNIVERSITY  
of MANCHESTER



# Early Output Logic using Anti-Tokens

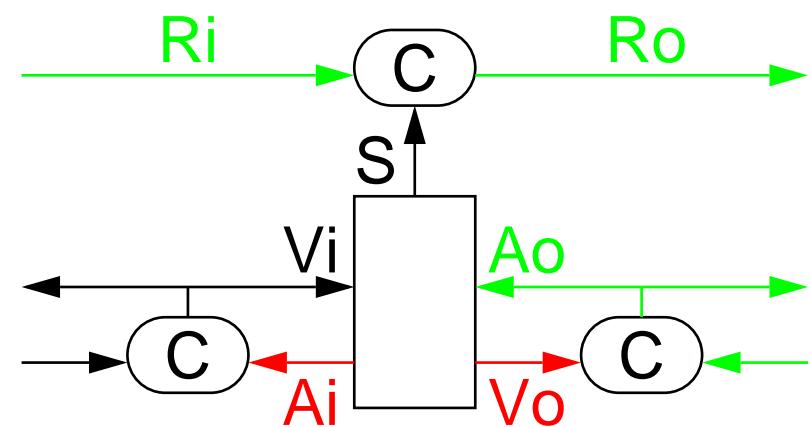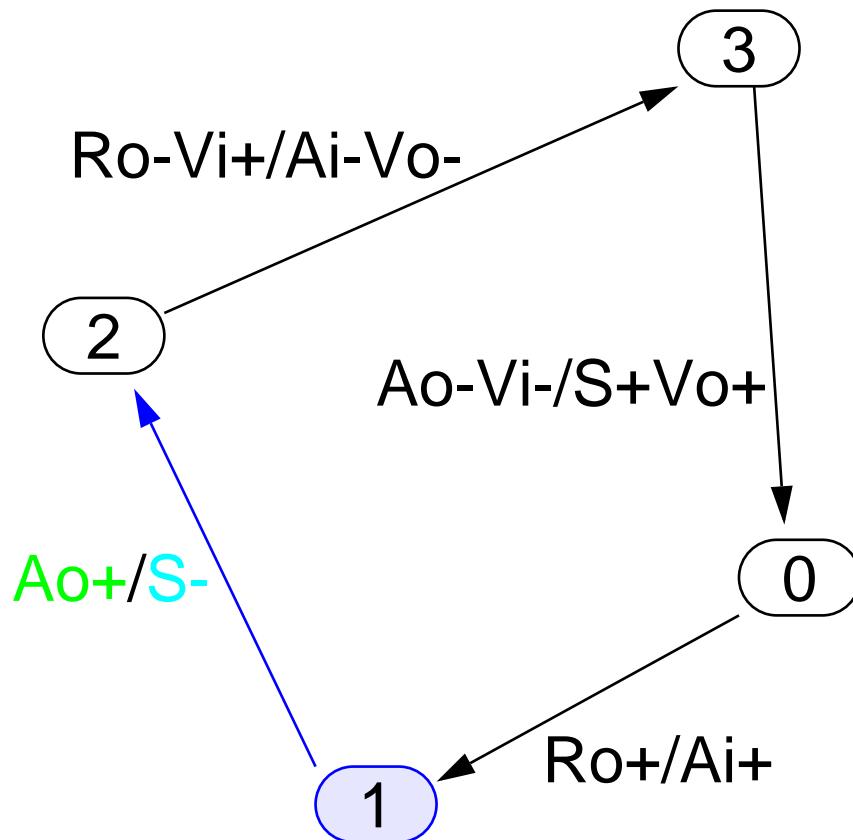



# Early Output Logic using Anti-Tokens

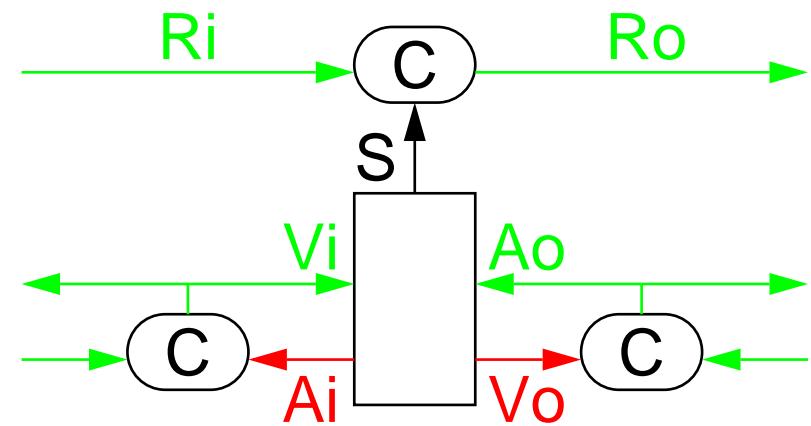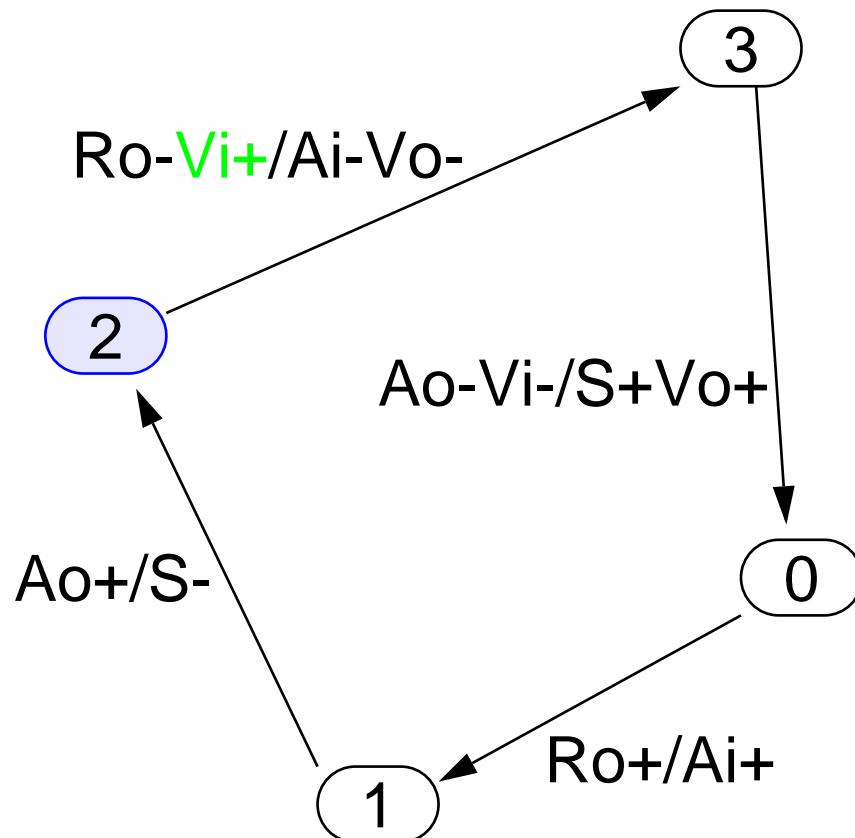



# Early Output Logic using Anti-Tokens

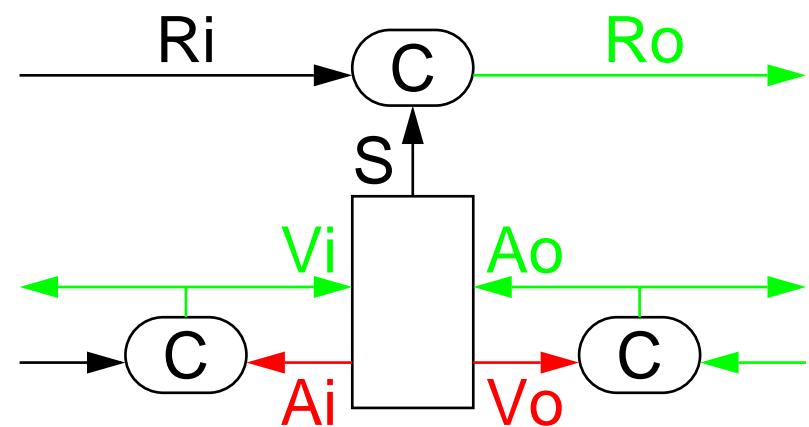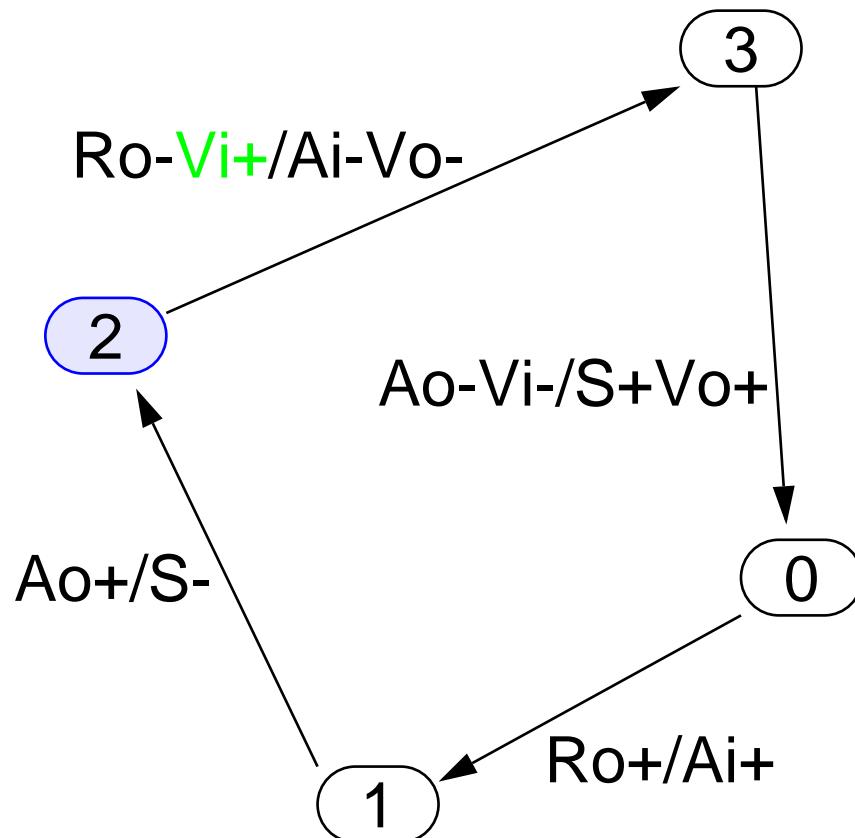



# Early Output Logic using Anti-Tokens

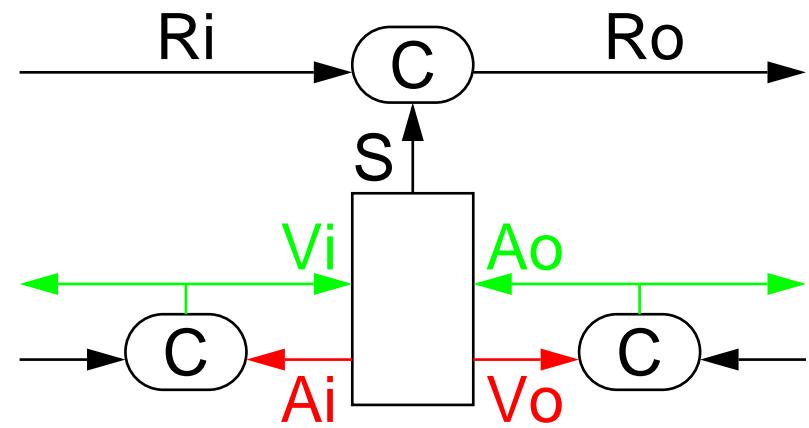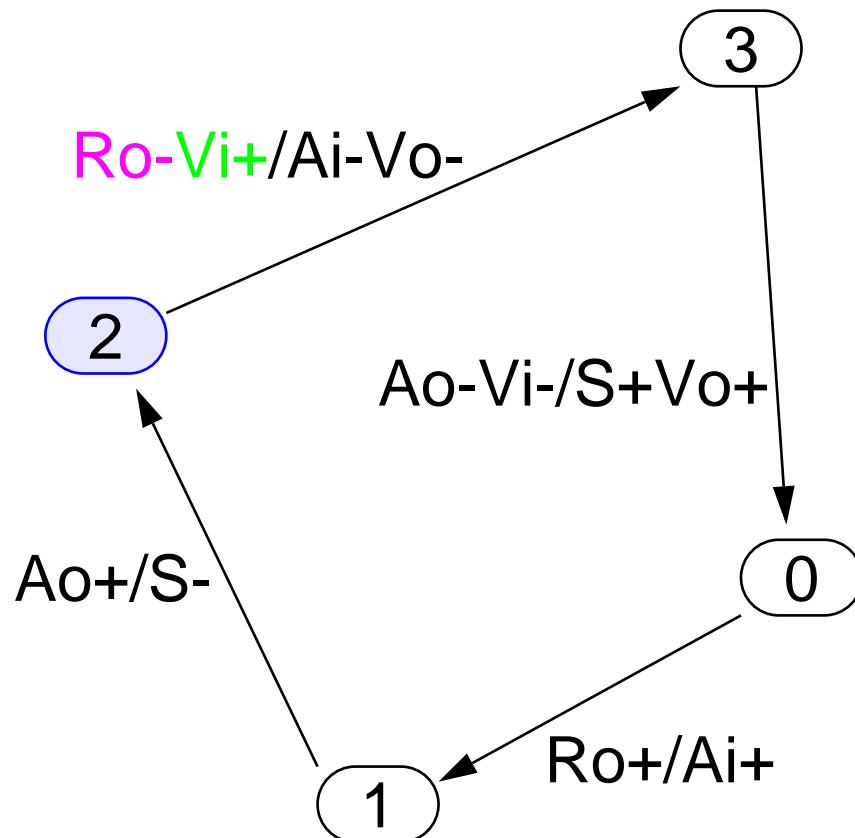



# Early Output Logic using Anti-Tokens

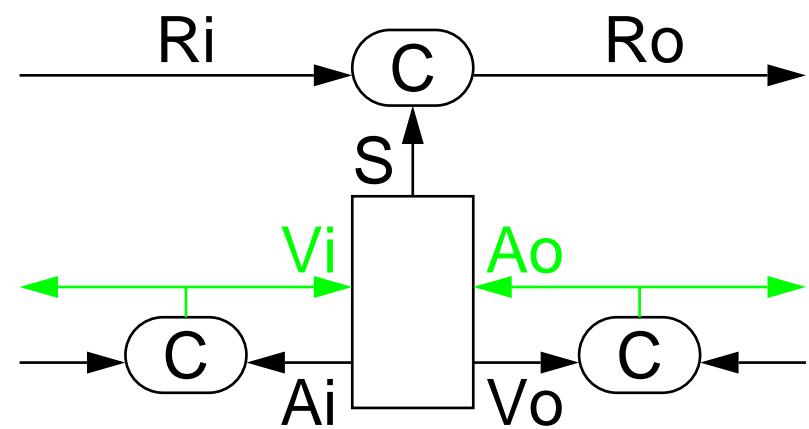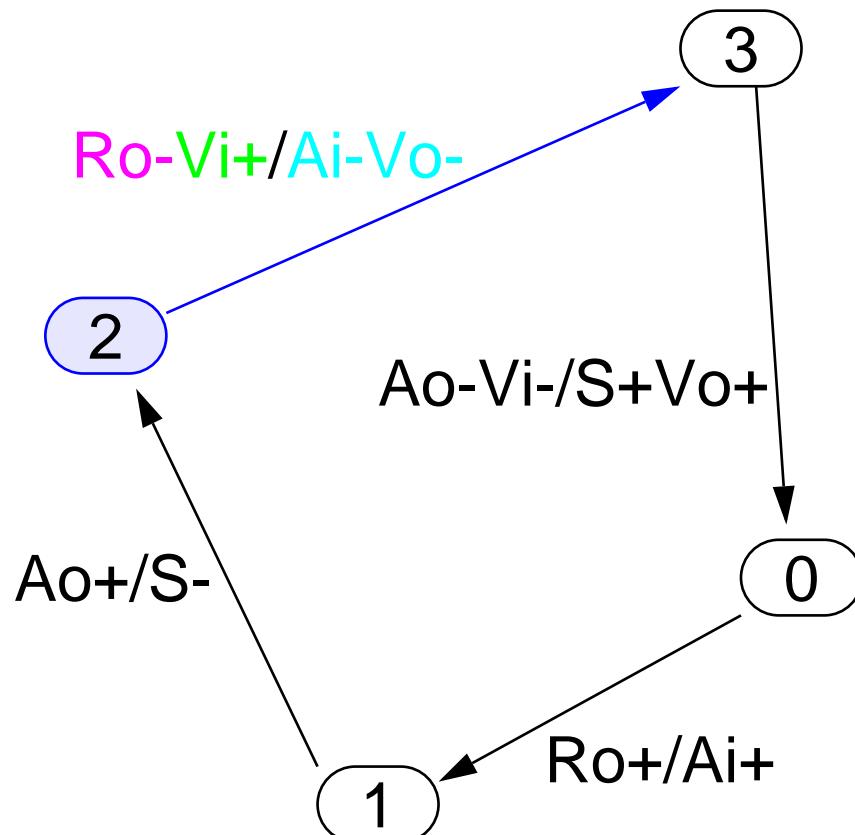



# Early Output Logic using Anti-Tokens

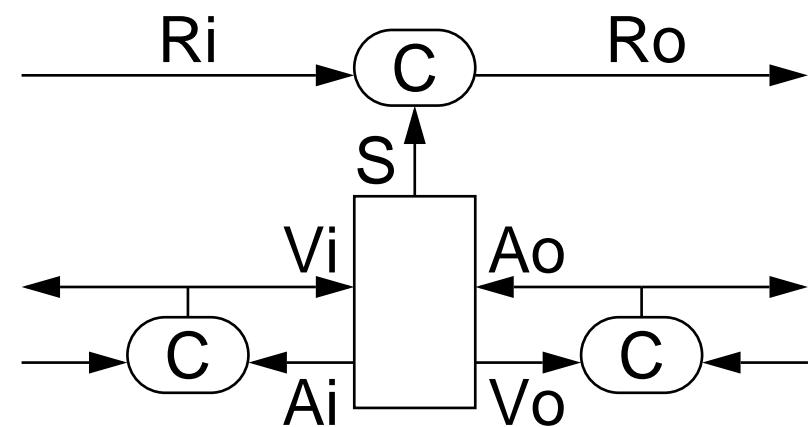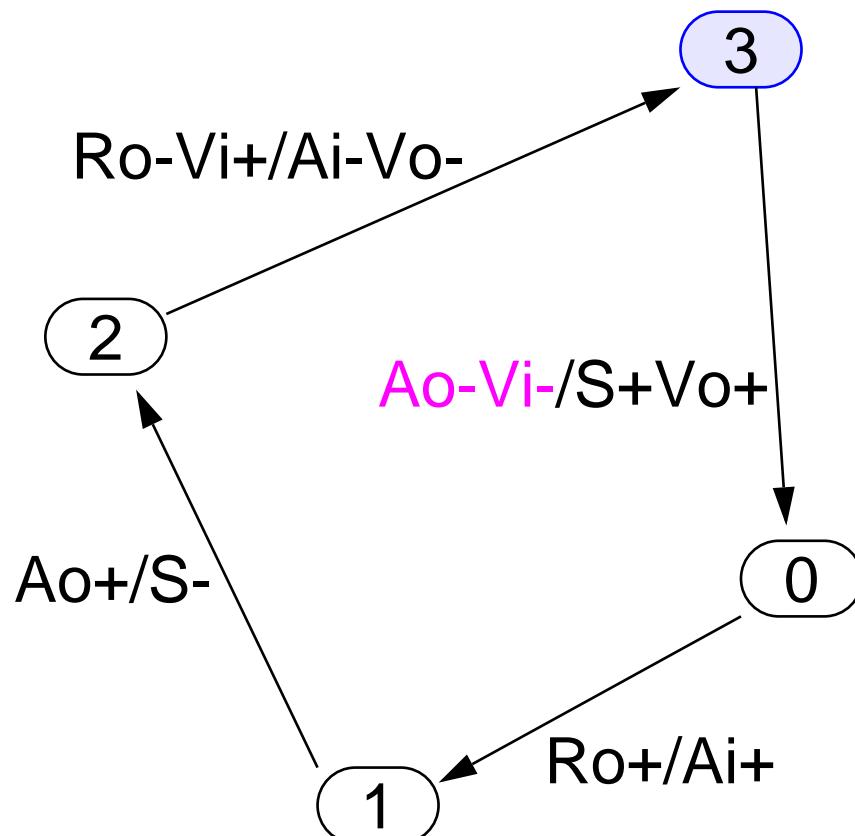


# Early Output Logic using Anti-Tokens

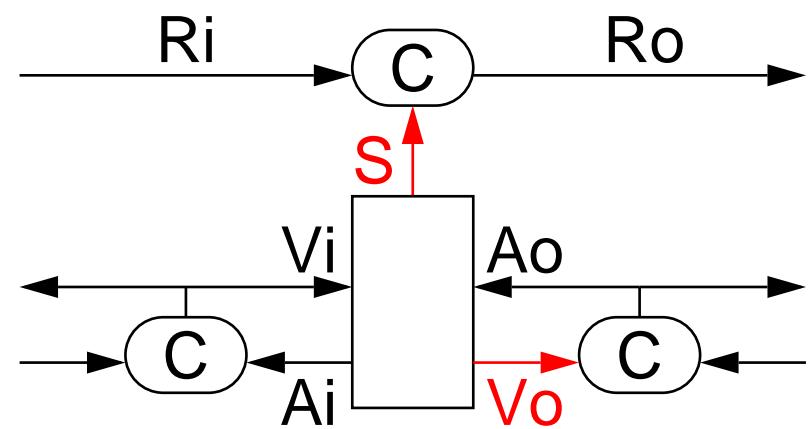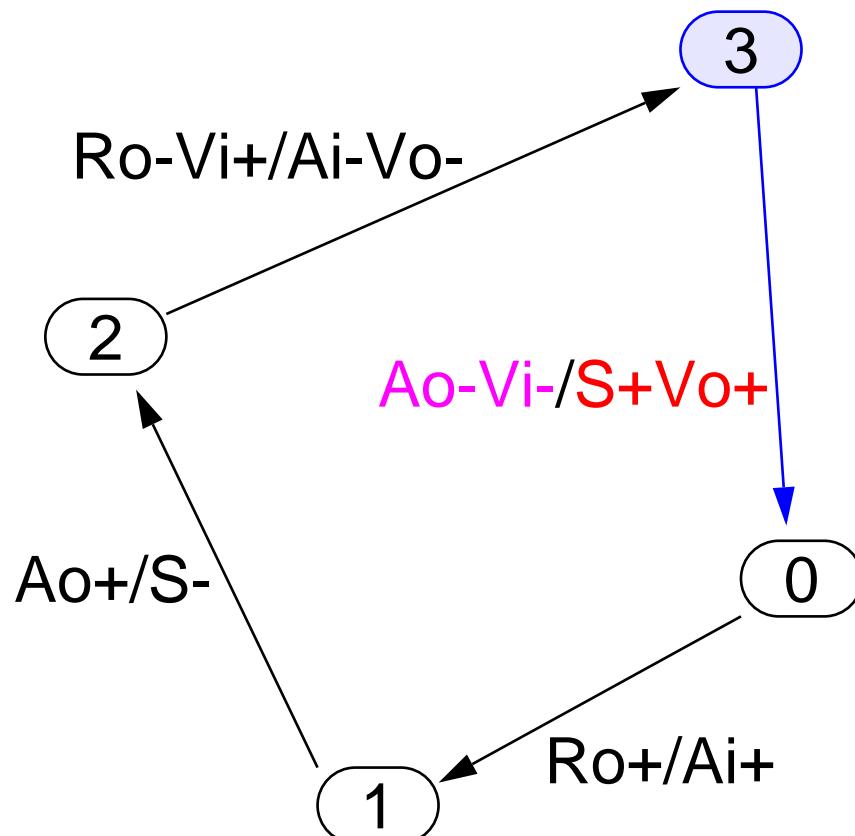


# Early Output Logic using Anti-Tokens

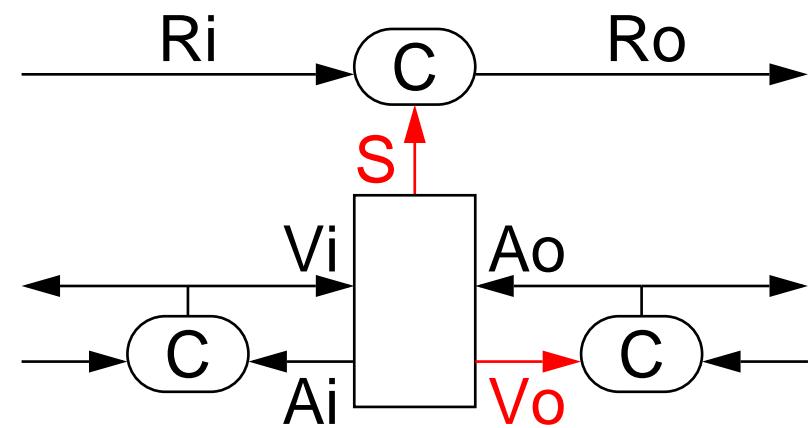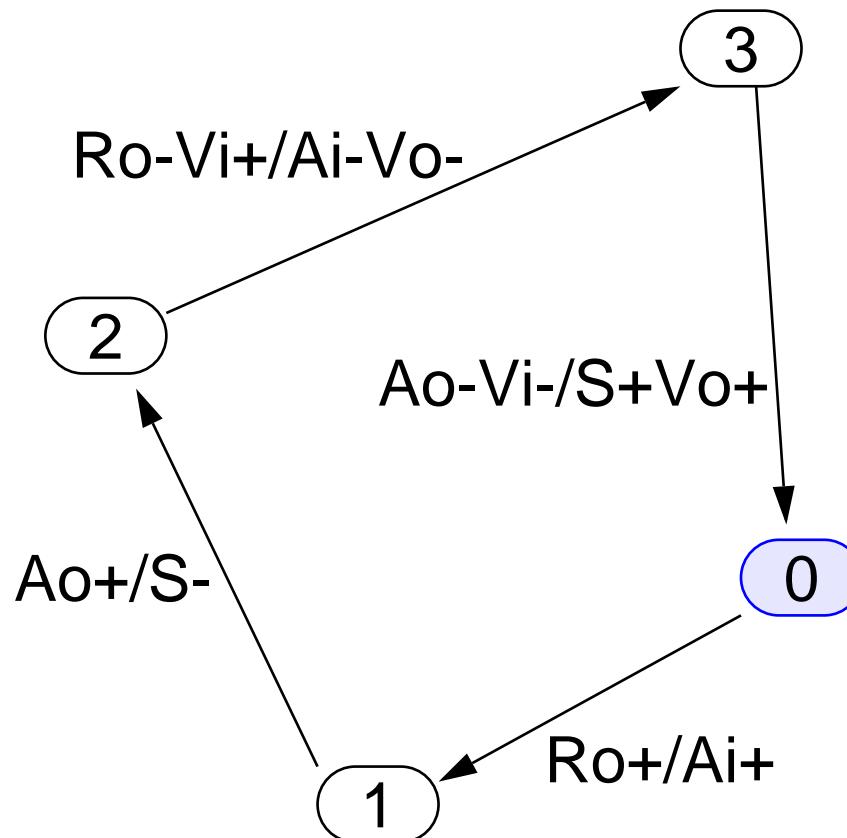


# Early Output Logic using Anti-Tokens

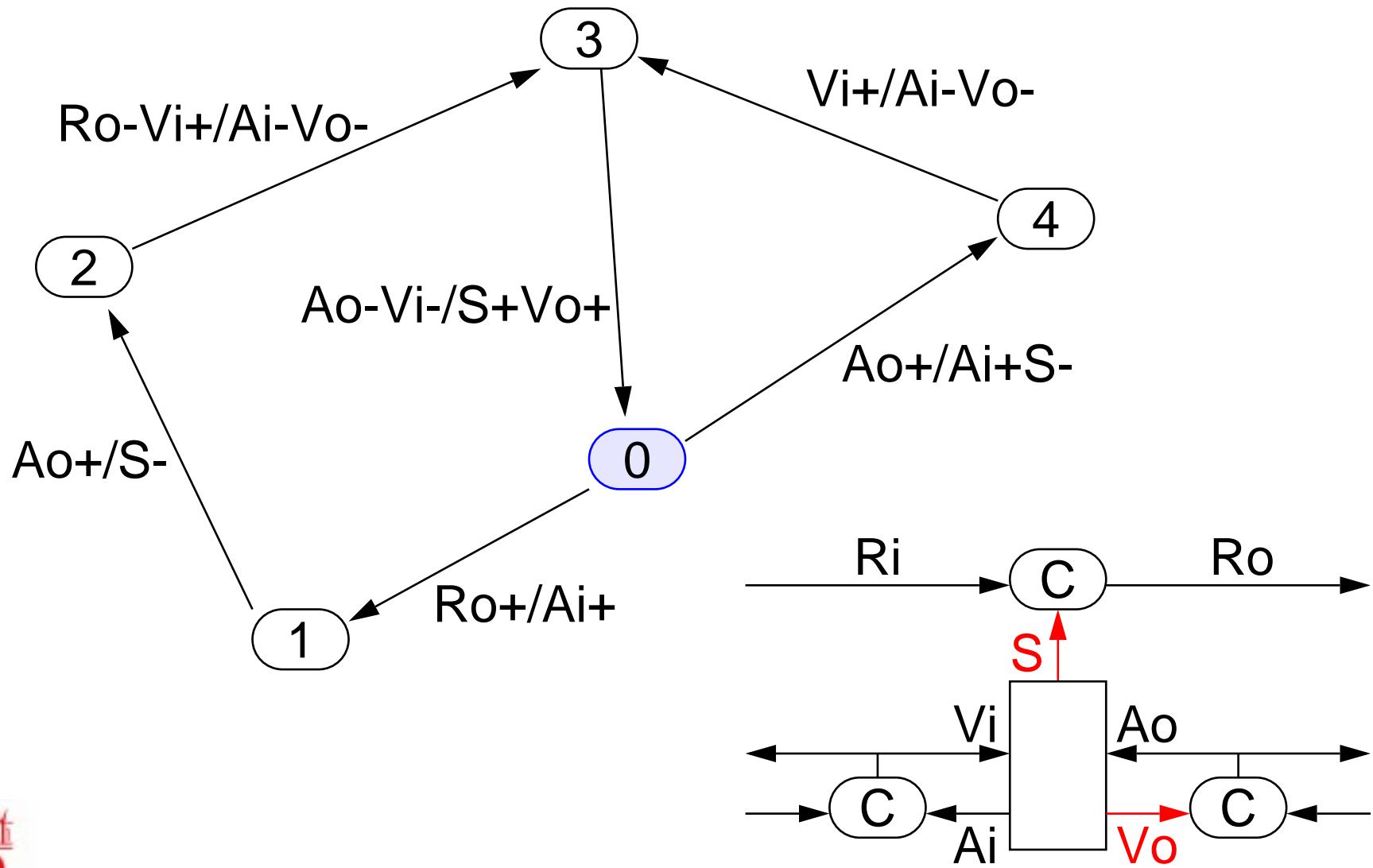


# Early Output Logic using Anti-Tokens

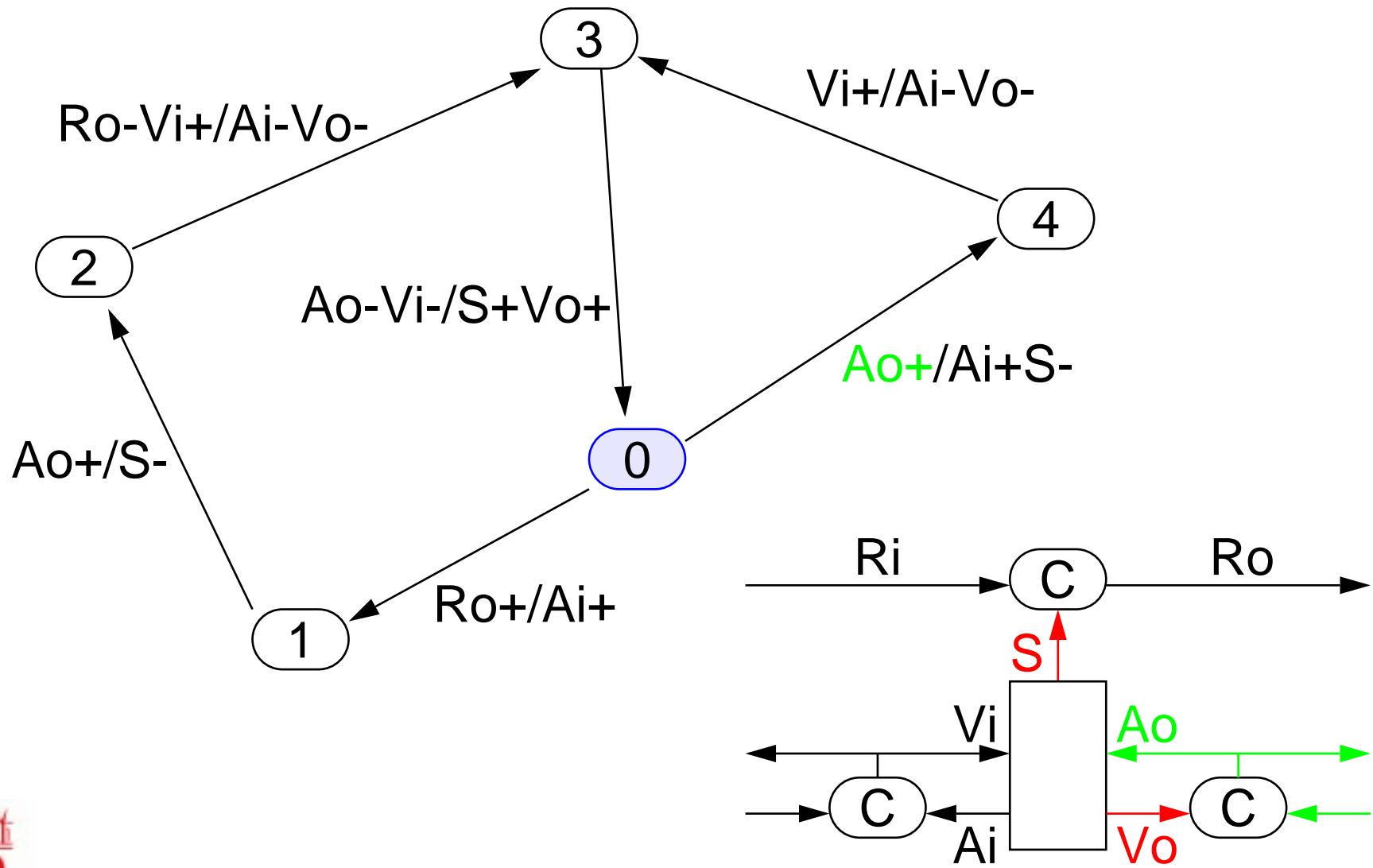

# Early Output Logic using Anti-Tokens

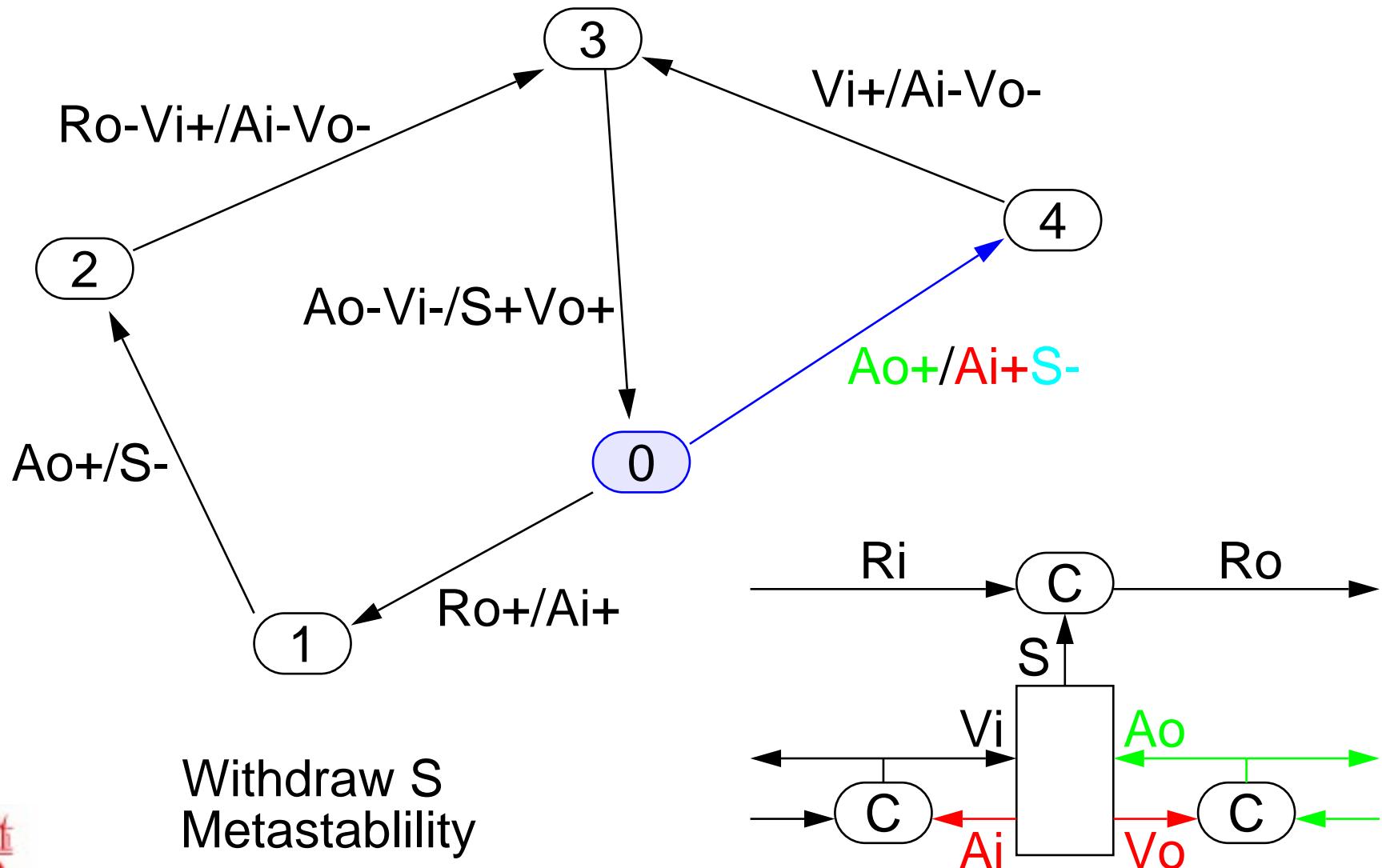


# Early Output Logic using Anti-Tokens

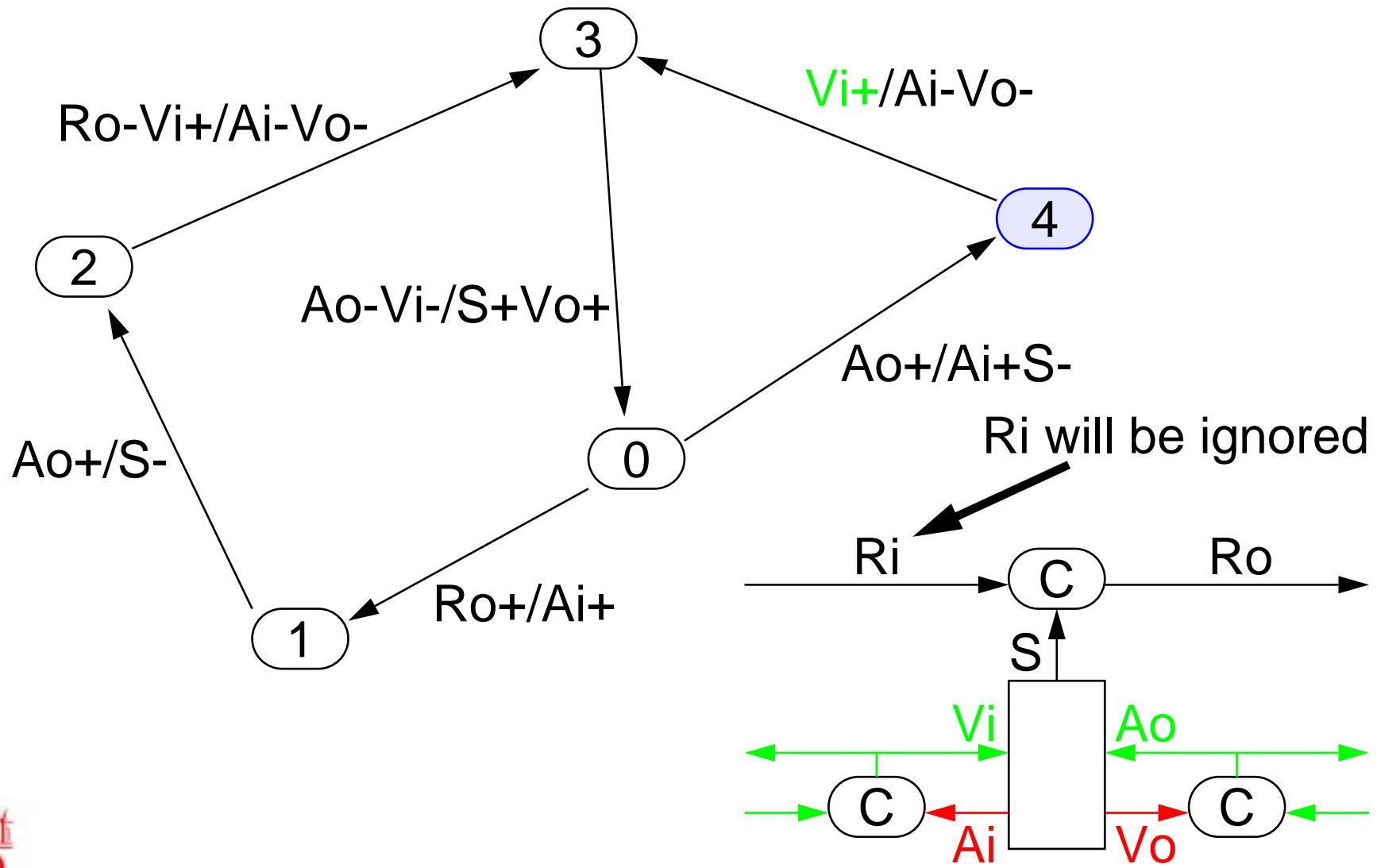


THE UNIVERSITY  
of MANCHESTER

# Early Output Logic using Anti-Tokens

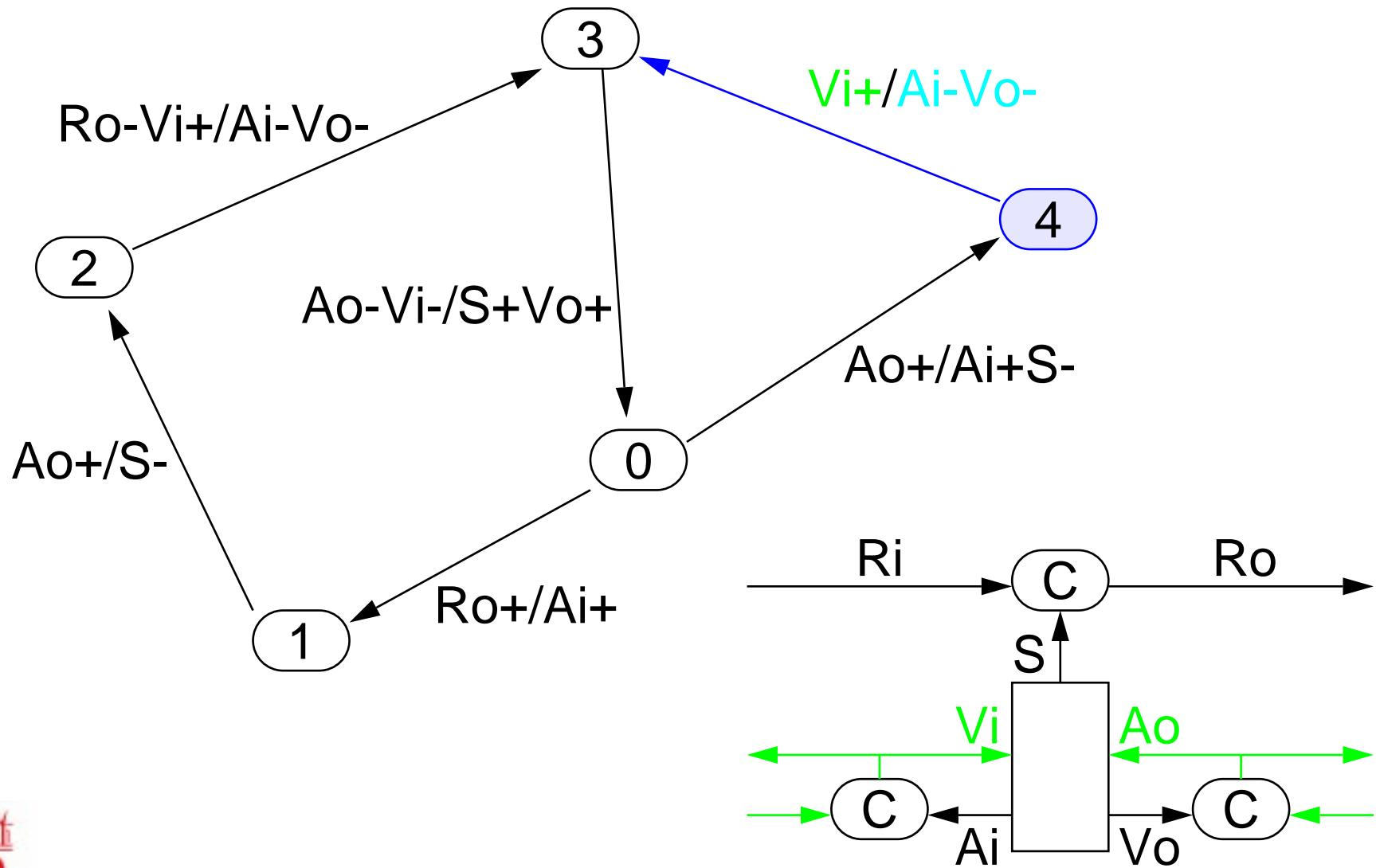


# Early Output Logic using Anti-Tokens

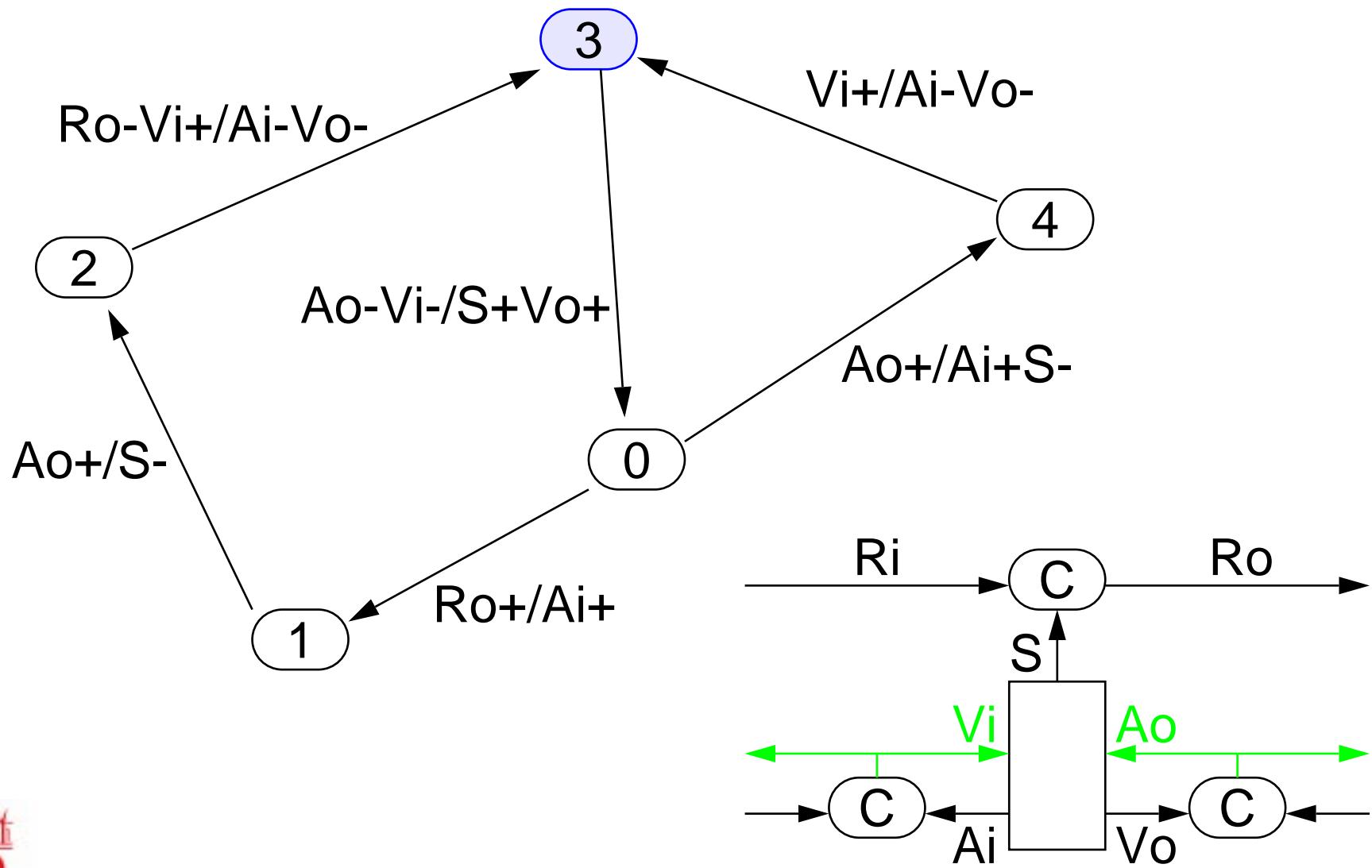


THE UNIVERSITY  
of MANCHESTER

# Early Output Logic using Anti-Tokens

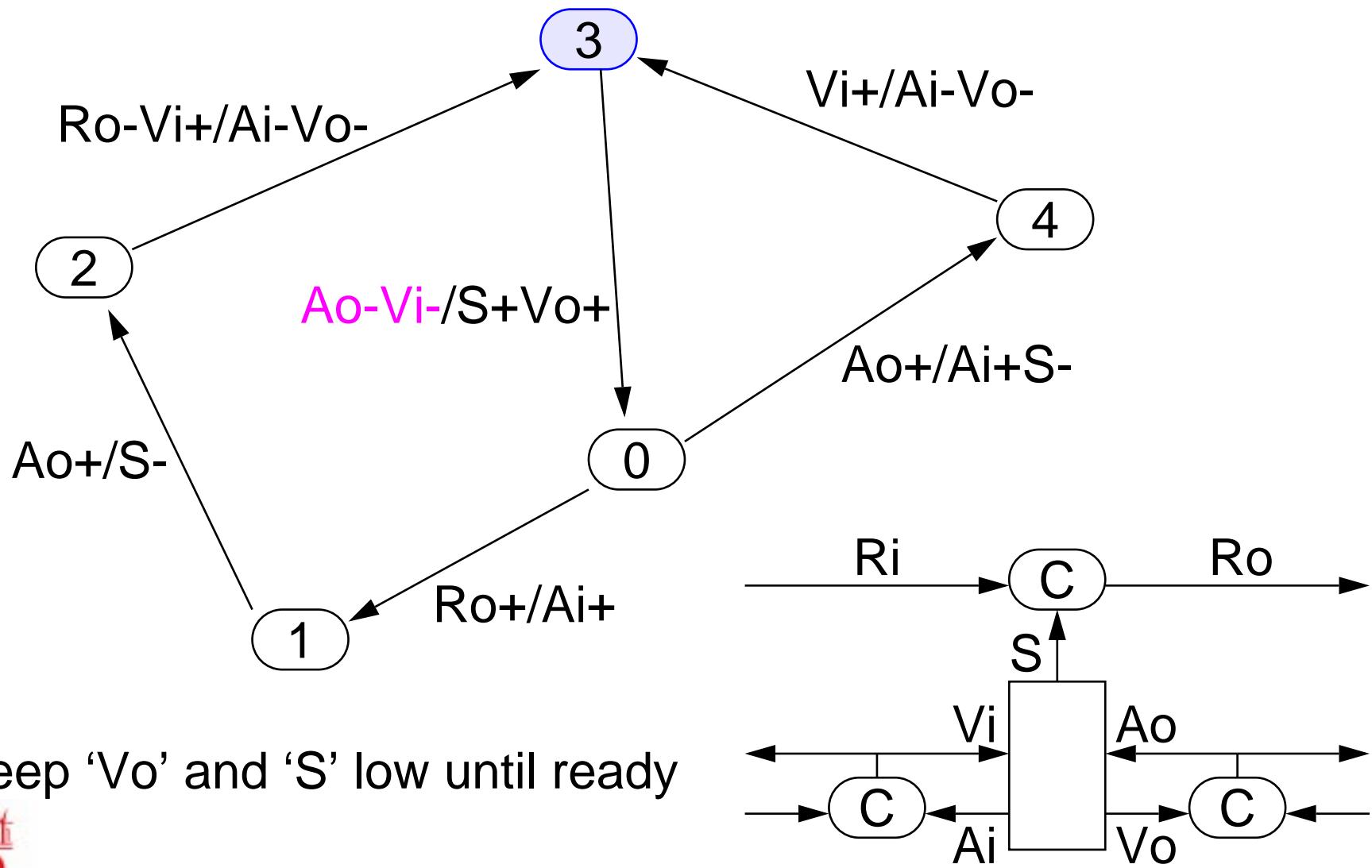


THE UNIVERSITY  
of MANCHESTER

# Early Output Logic using Anti-Tokens

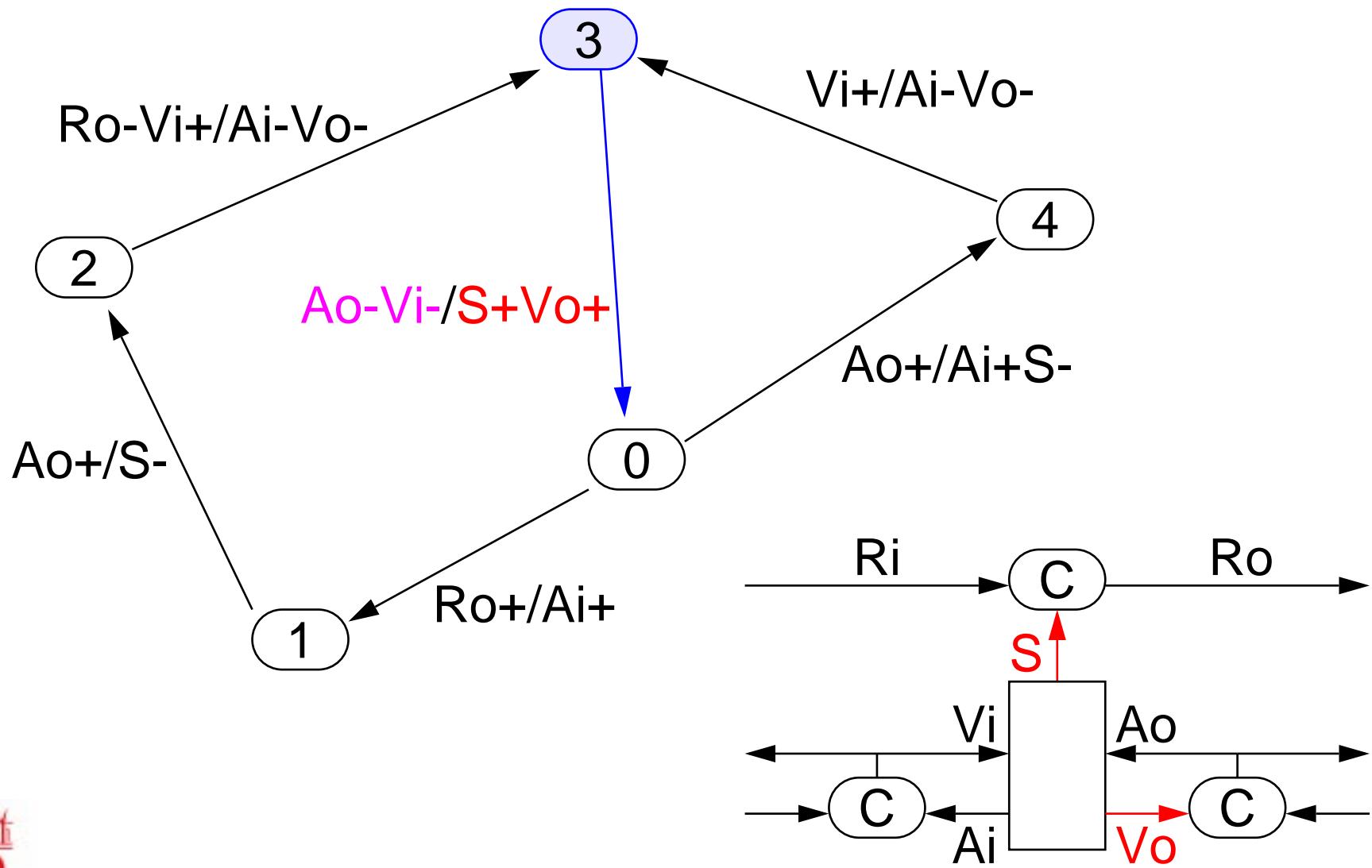

# Early Output Logic using Anti-Tokens

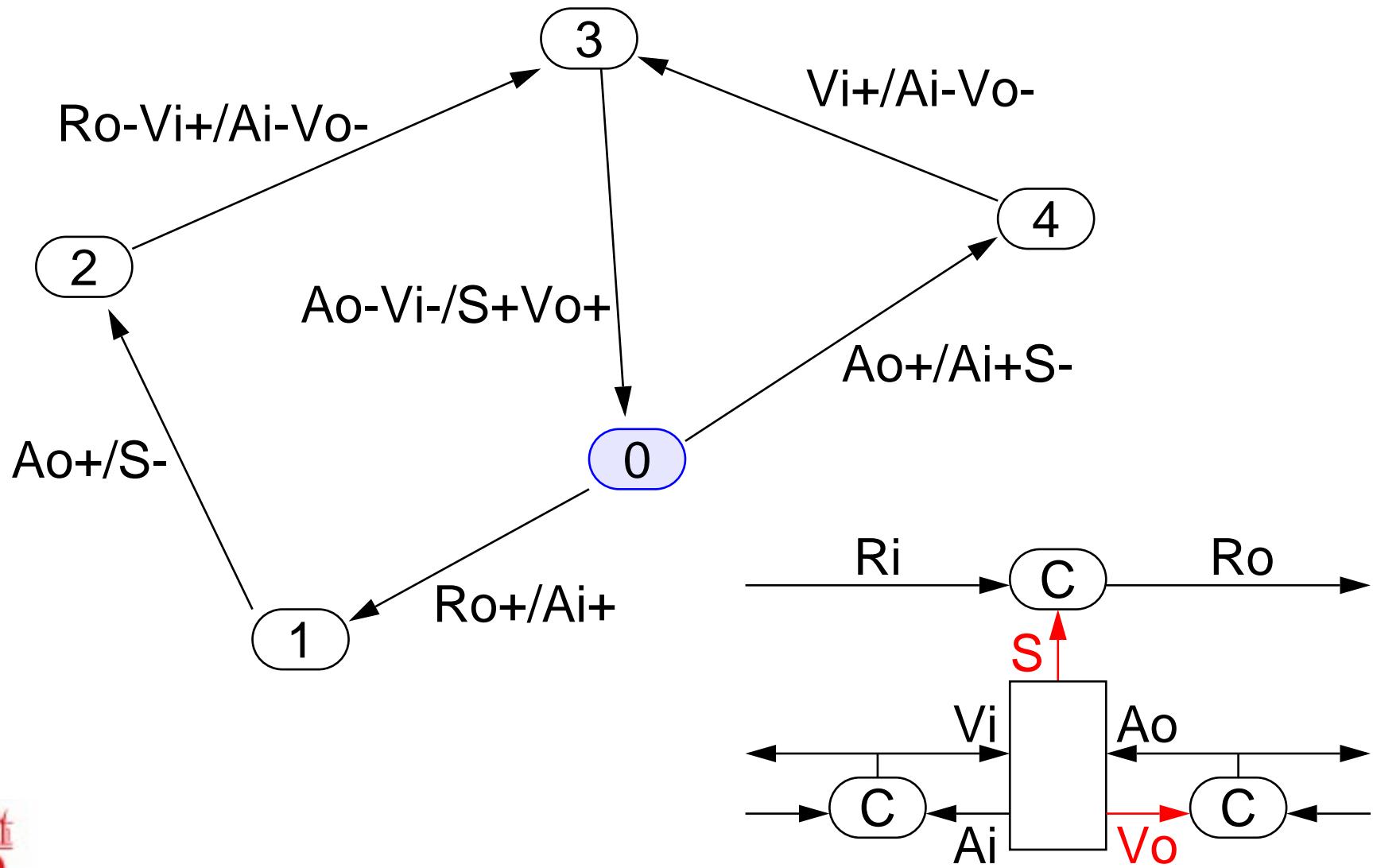

## Summary

- Early output logic

- Early output cases

- Better semi-decoupled latches

- Remove synchronisation

- Anti-tokens

- Arbiter free



THE UNIVERSITY  
of MANCHESTER